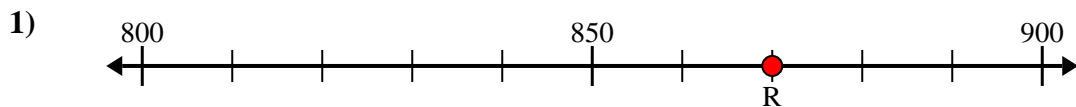





Find the value of R.


Answers




1. _____

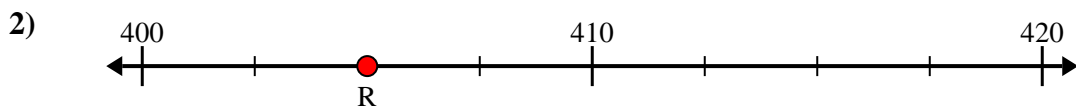


2. _____

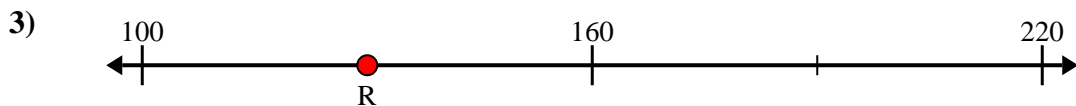


3. _____

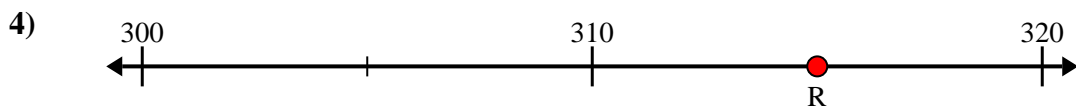


4. _____

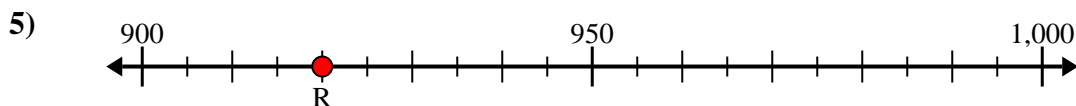


5. _____

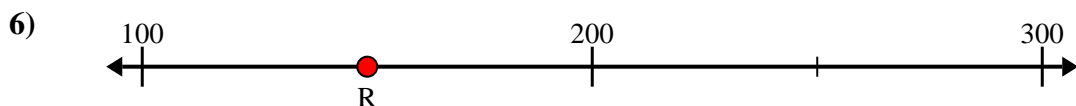


6. _____

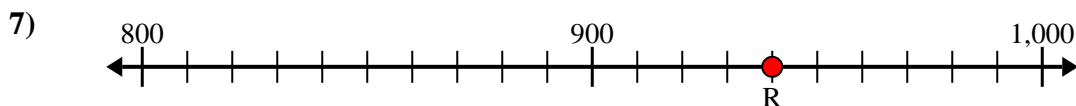


7. _____

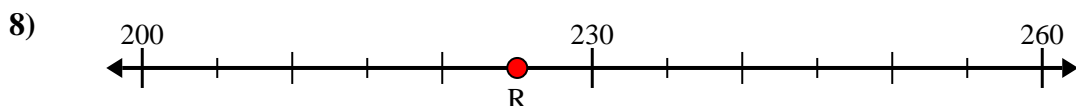

8. _____

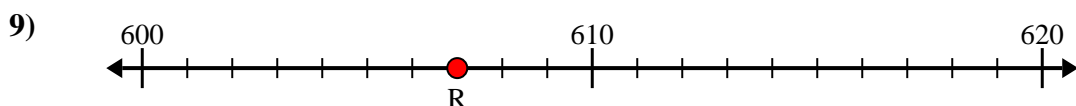











9. _____

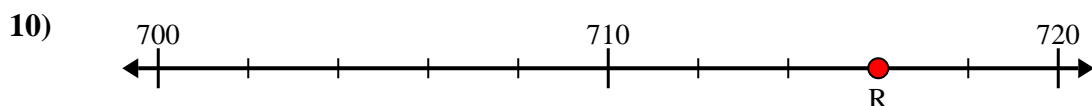

10. _____



Find the value of R.

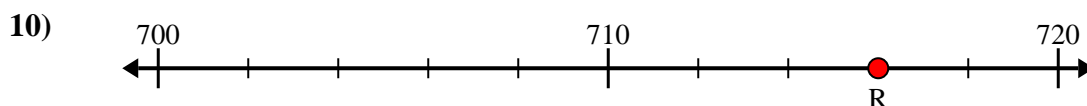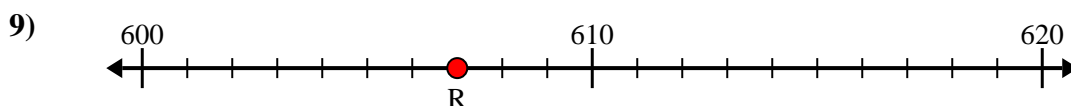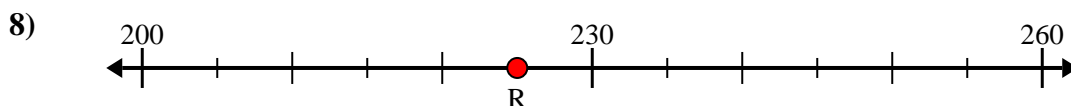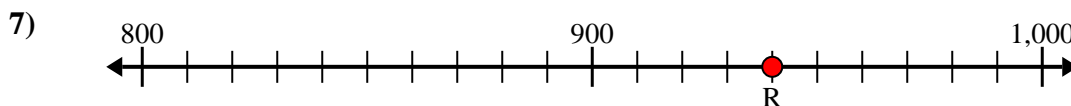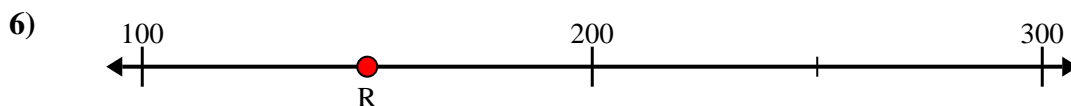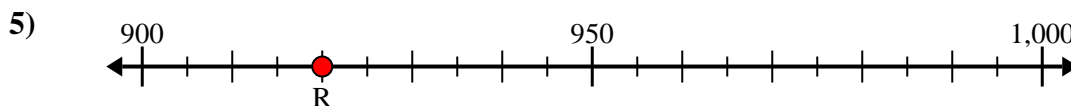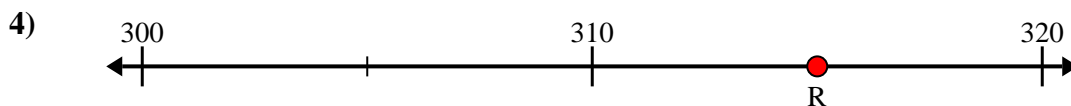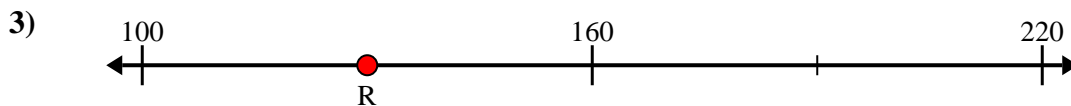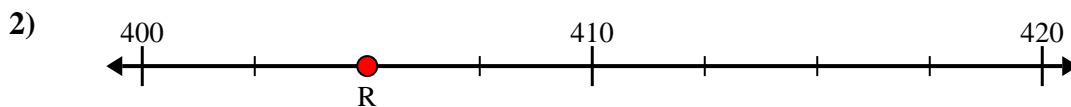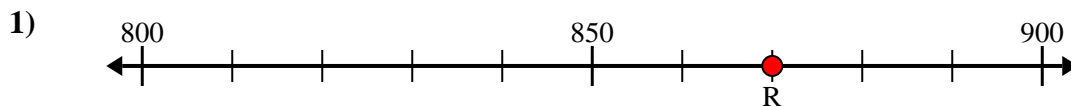**Answers**1. 8702. 4053. 1304. 3155. 9206. 1507. 9408. 2259. 60710. 716