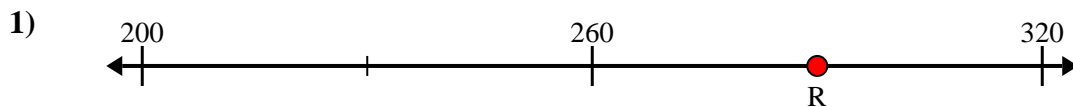





Find the value of R.


Answers




1. \_\_\_\_\_

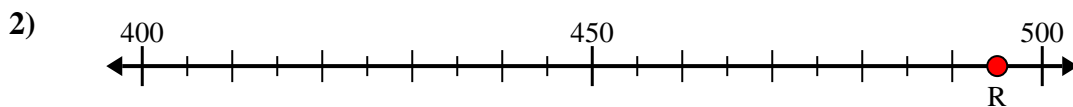


2. \_\_\_\_\_

 


3. \_\_\_\_\_

 


4. \_\_\_\_\_

 


5. \_\_\_\_\_

 


6. \_\_\_\_\_

 


7. \_\_\_\_\_

 

8. \_\_\_\_\_

 











9. \_\_\_\_\_

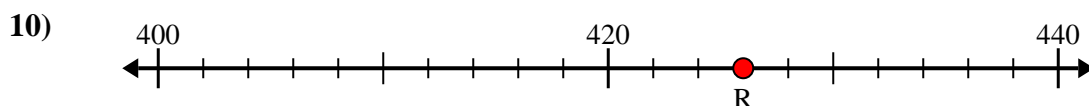

10. \_\_\_\_\_



Find the value of R.

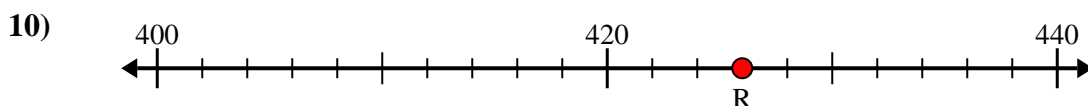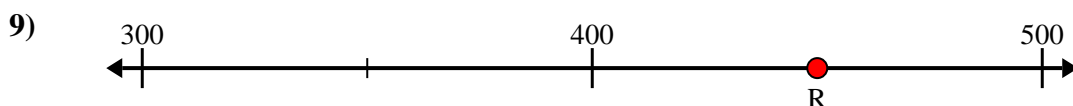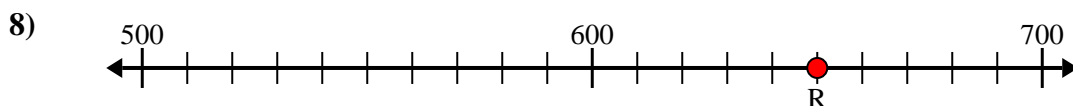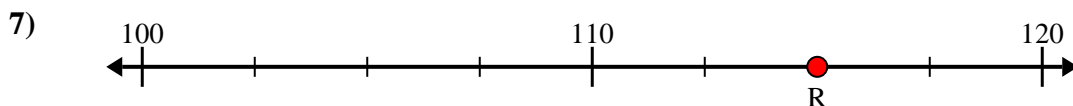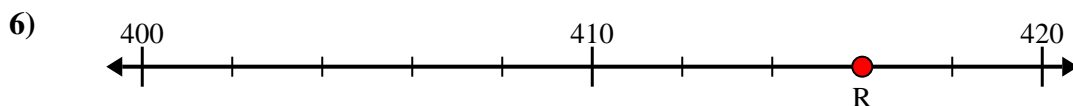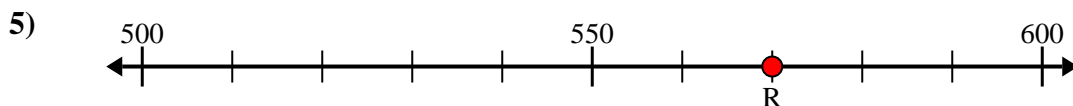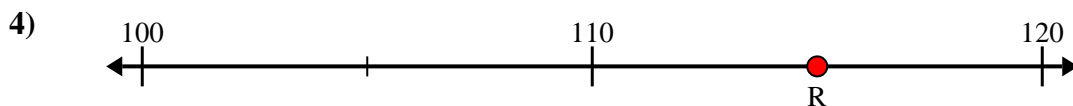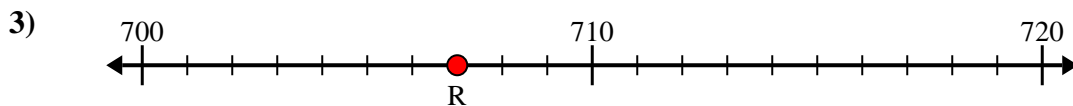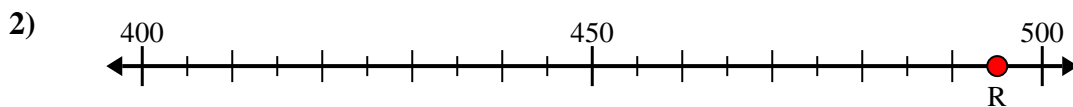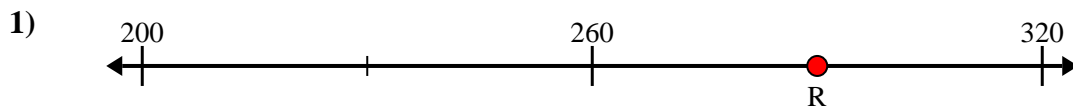

Answers

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650

9. 450

10. 426