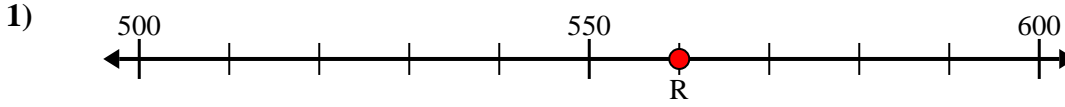





Find the value of R.


Answers




1. _____

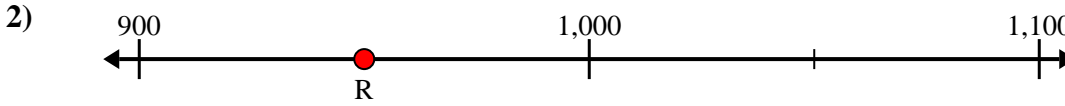


2. _____

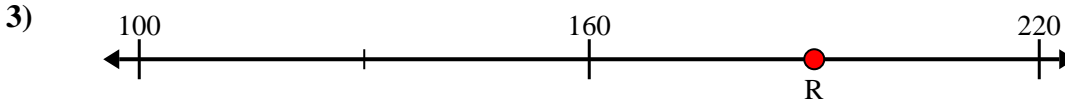


3. _____

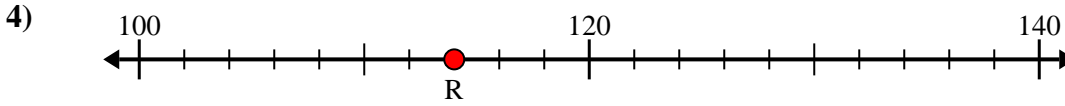


4. _____

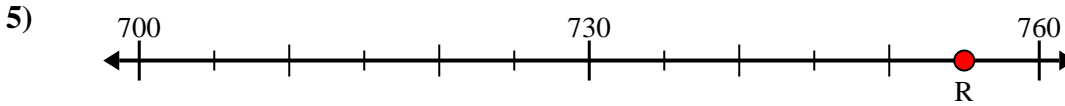


5. _____

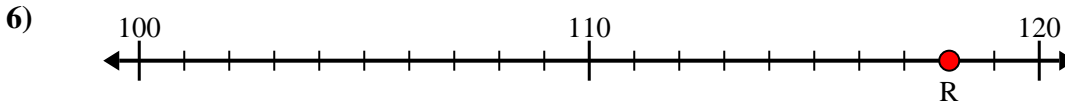


6. _____

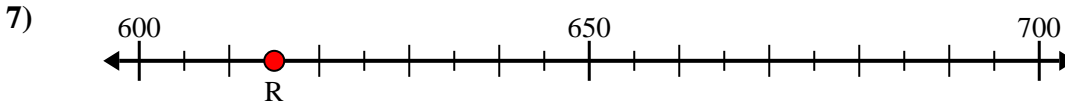


7. _____

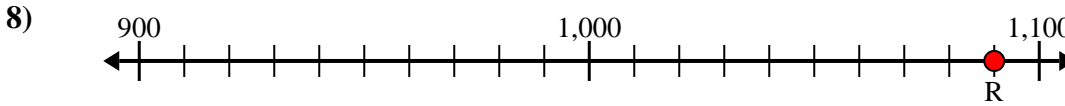

8. _____

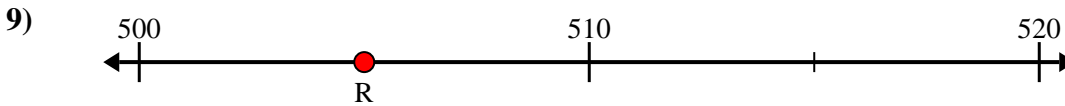











9. _____

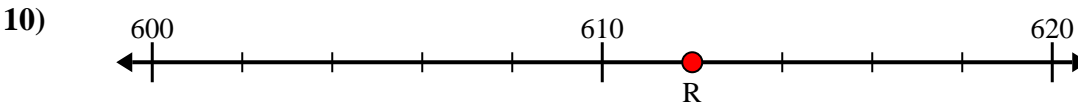

10. _____



Find the value of R.

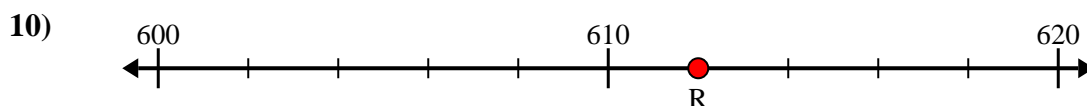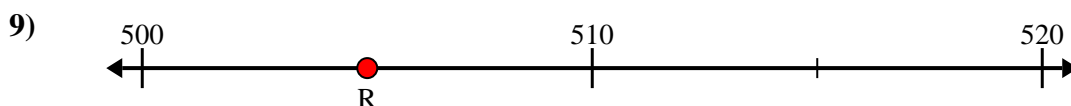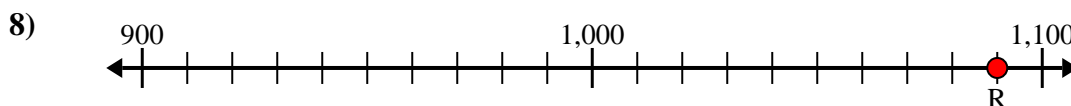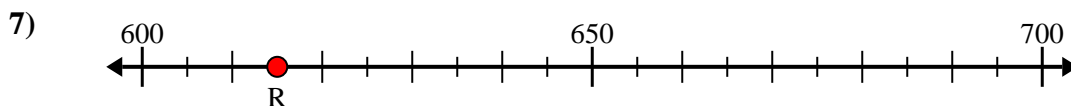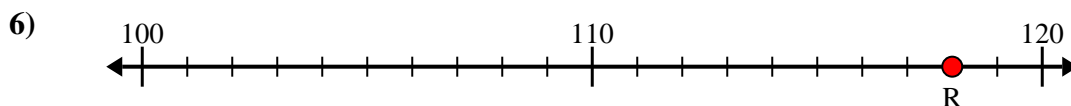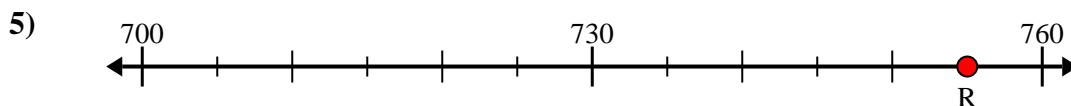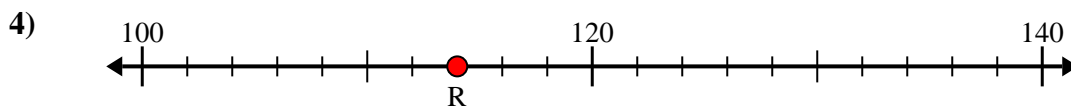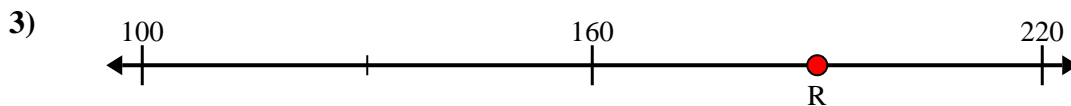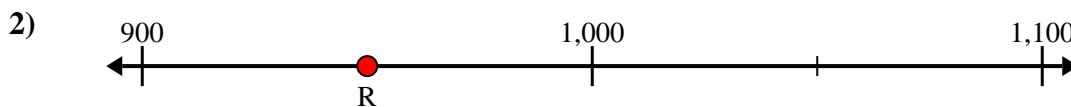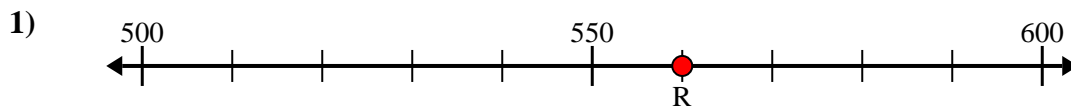**Answers**1. 5602. 9503. 1904. 1145. 7556. 1187. 6158. 1,0909. 50510. 612