

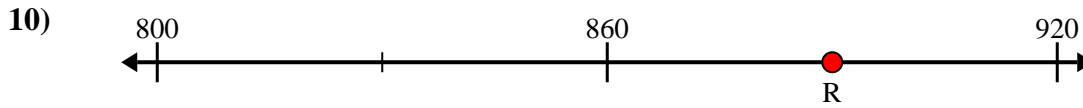
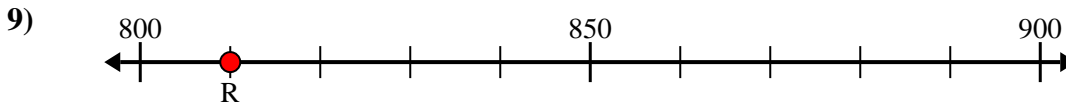
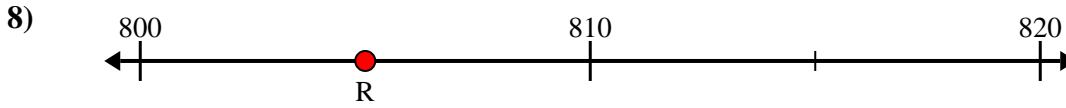
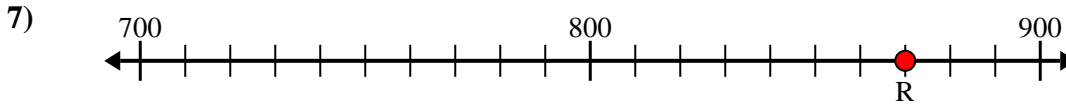
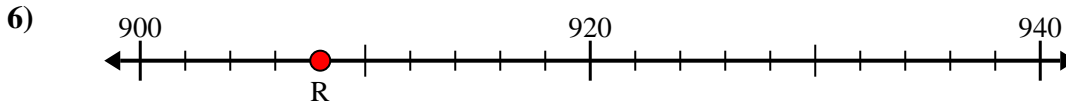
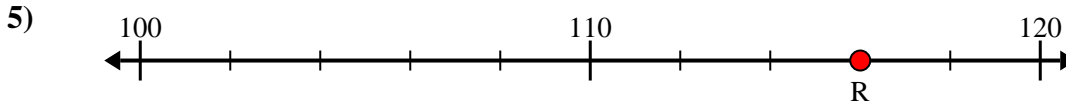
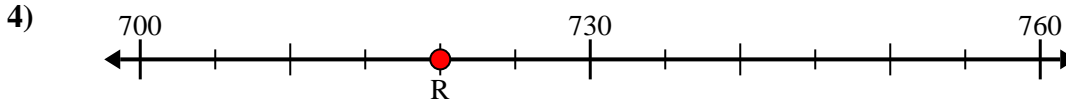
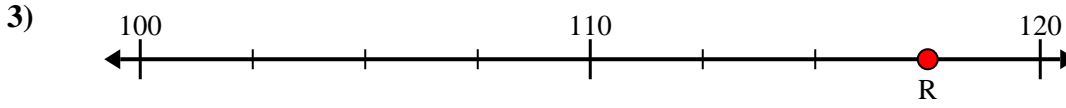


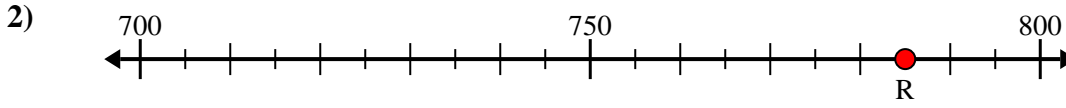

Find the value of R.










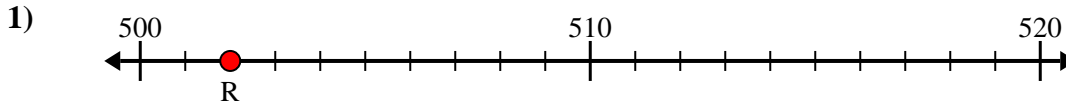


Answers

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Find the value of R.

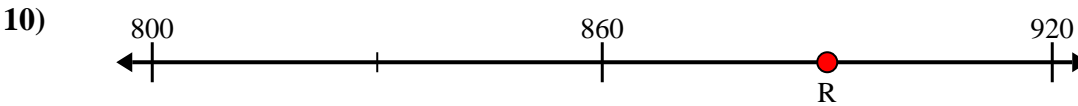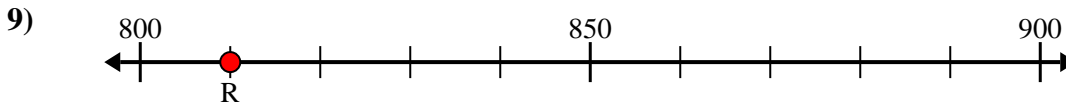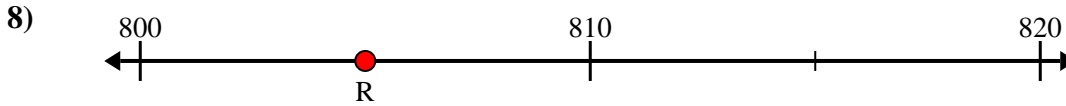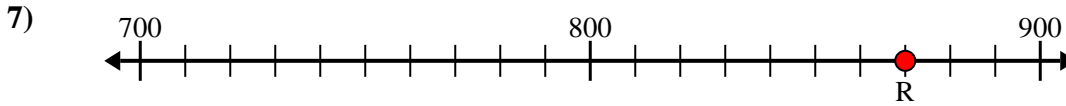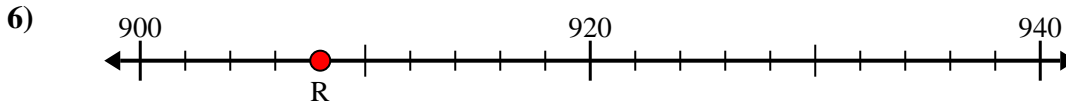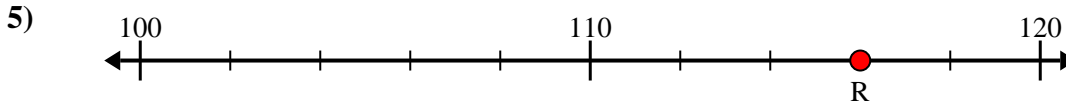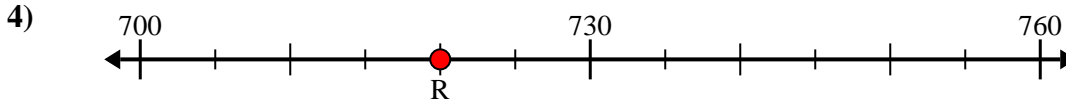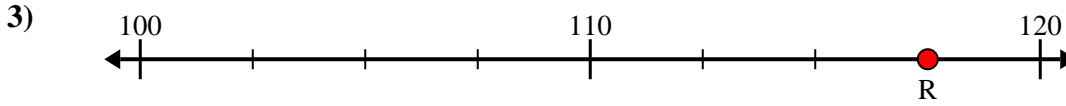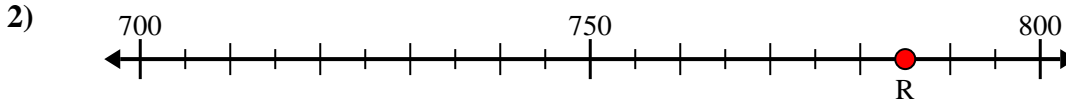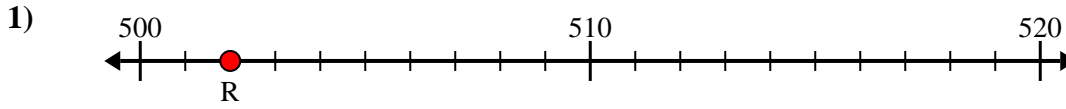

Answers

1. 502

2. 785

3. 117.5

4. 720

5. 116

6. 908

7. 870

8. 805

9. 810

10. 890