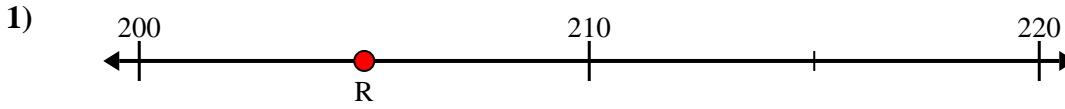





Find the value of R.


Answers




1. _____

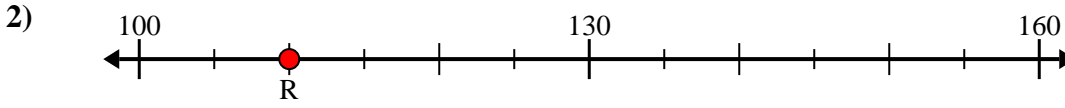


2. _____

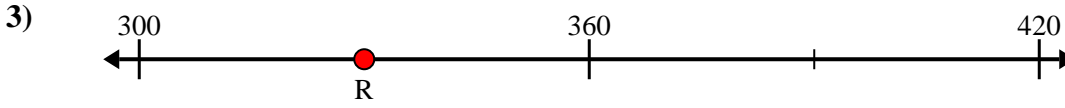


3. _____

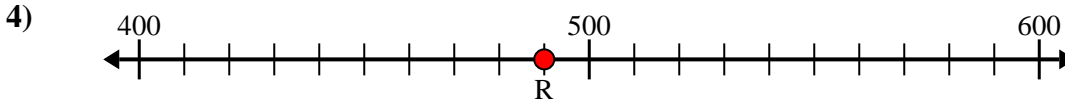


4. _____

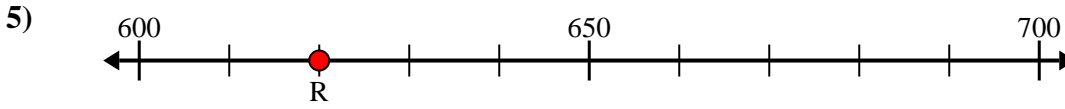


5. _____

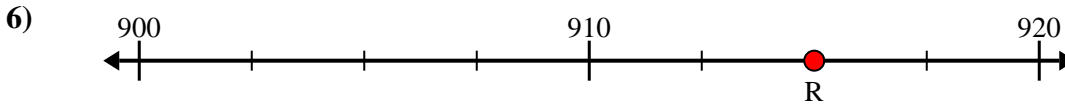


6. _____

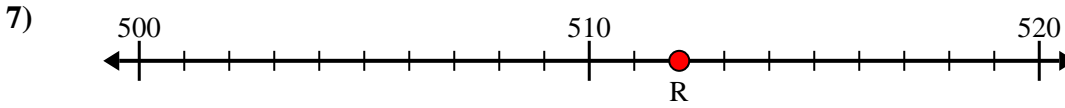


7. _____

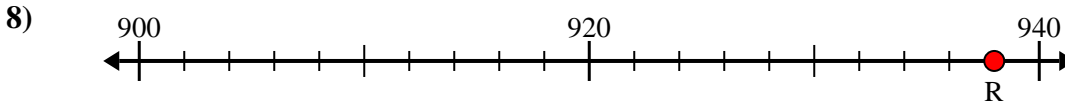

8. _____

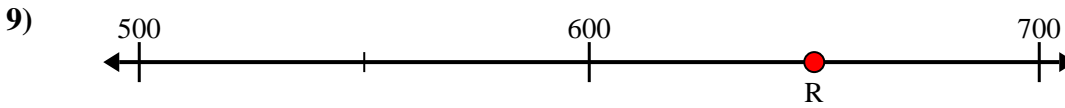











9. _____

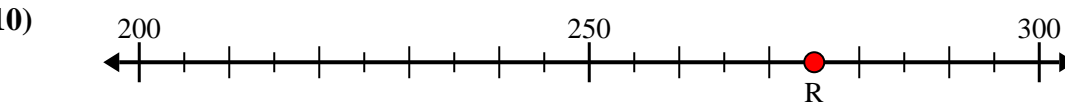

10. _____



Find the value of R.

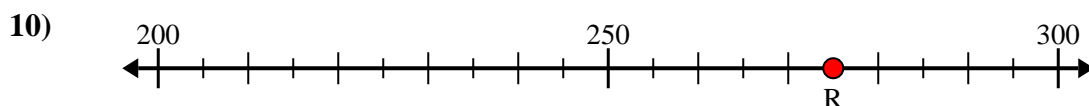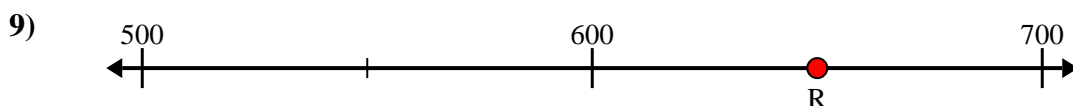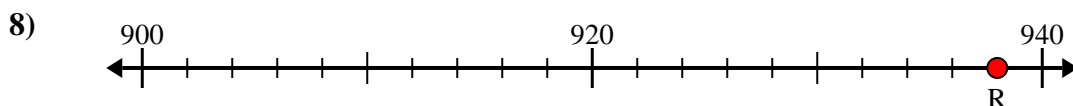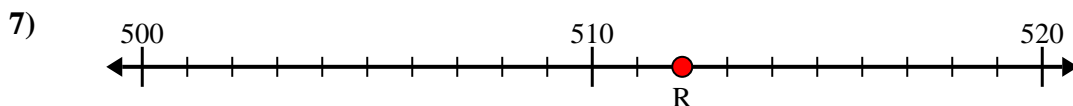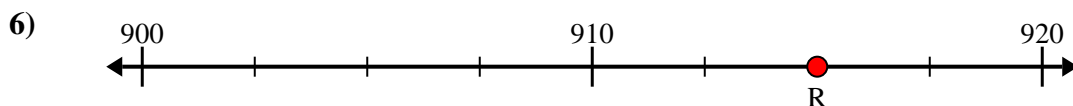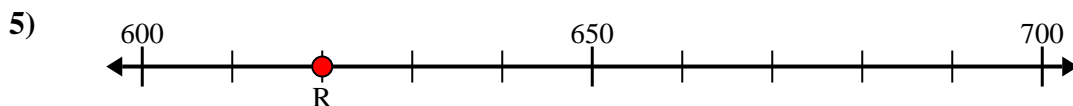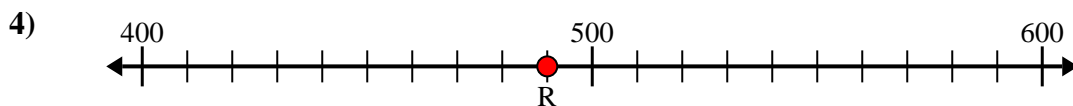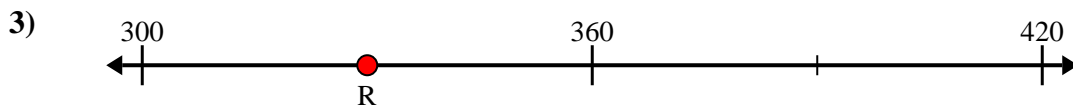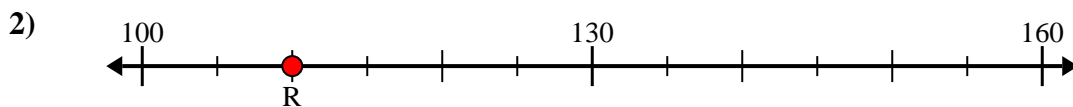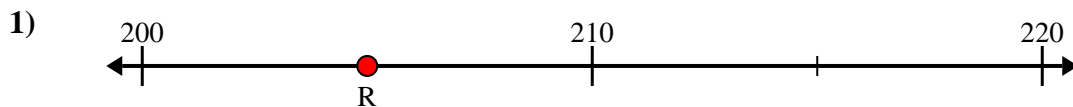

Answers

1. 205

2. 110

3. 330

4. 490

5. 620

6. 915

7. 512

8. 938


9. 650

10. 275



Find the value of R.


Answers

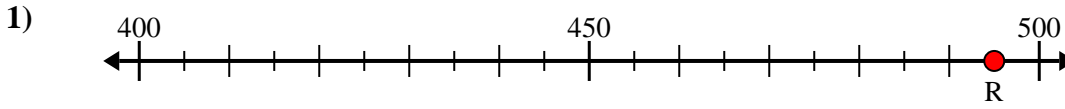


1. _____




2. _____

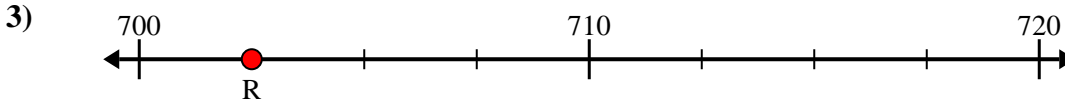


3. _____

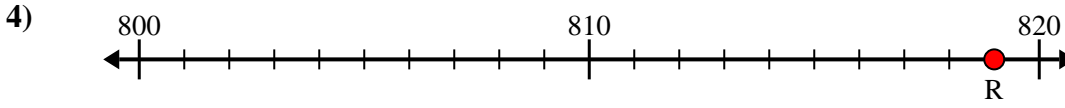

4. _____

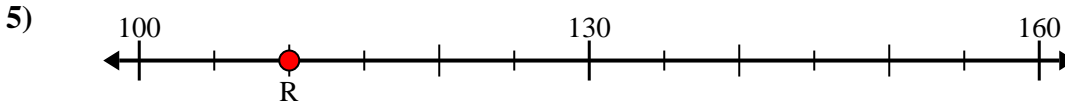


5. _____

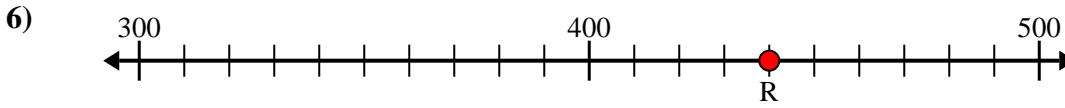


6. _____




7. _____

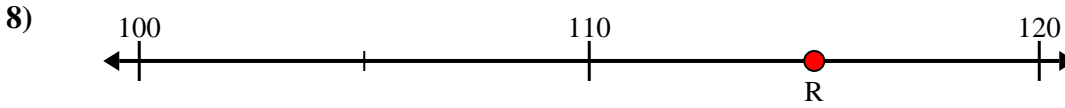

8. _____

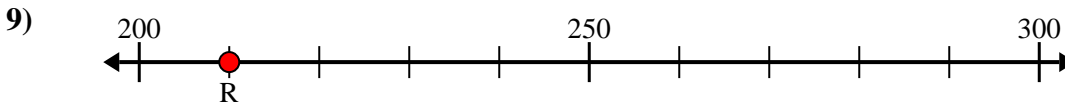











9. _____

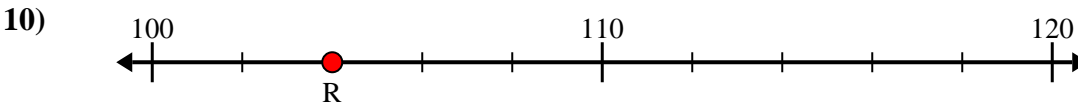

10. _____



Find the value of R.

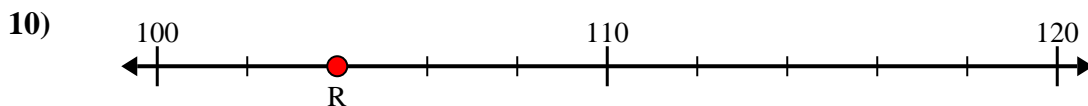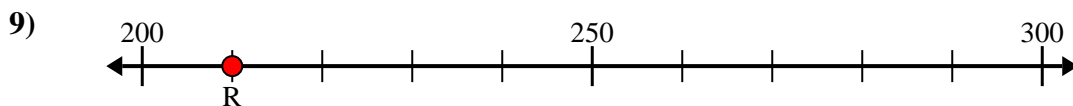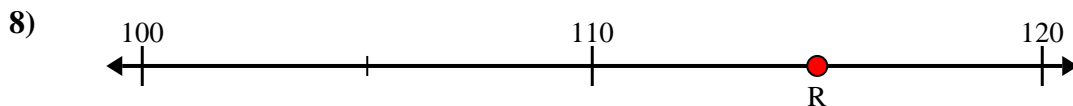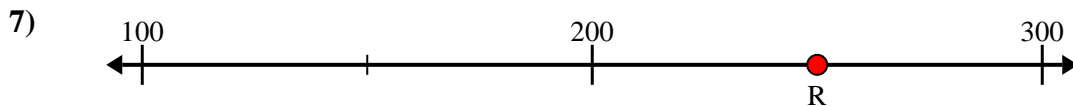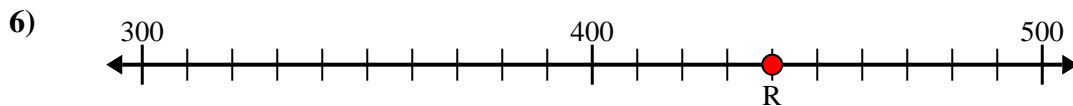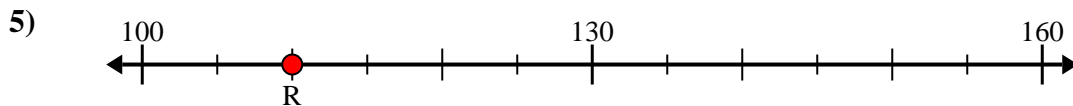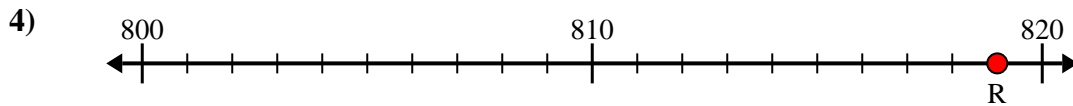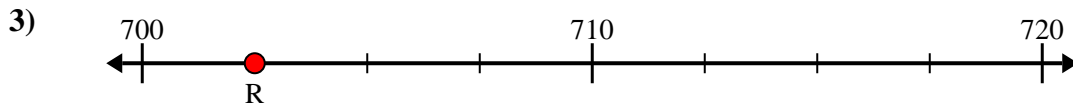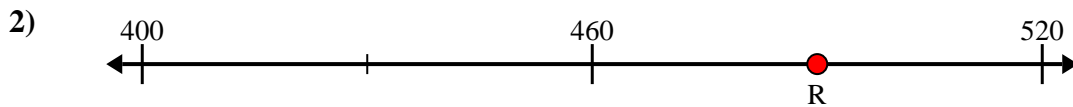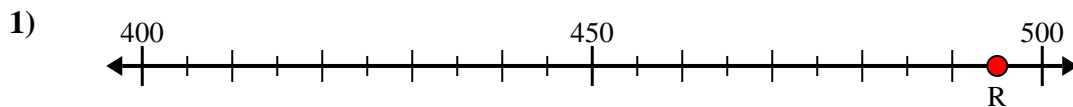

Answers

1. 495

2. 490

3. 702.5

4. 819

5. 110

6. 440

7. 250

8. 115


9. 210

10. 104




Find the value of R.


Answers

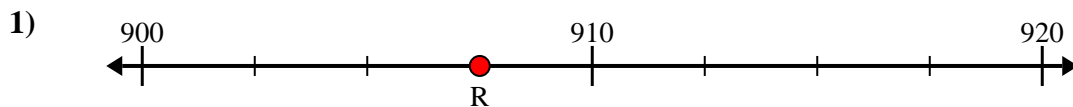


1. _____

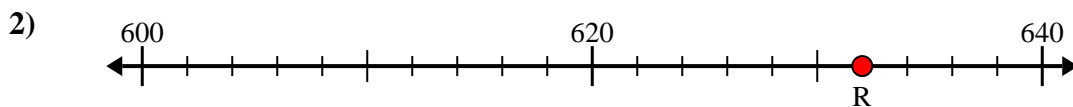


2. _____

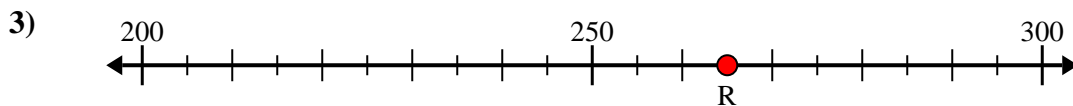


3. _____

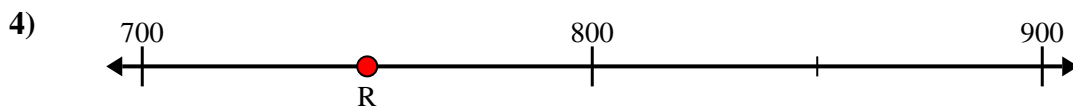


4. _____

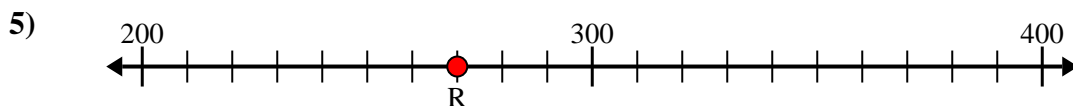


5. _____

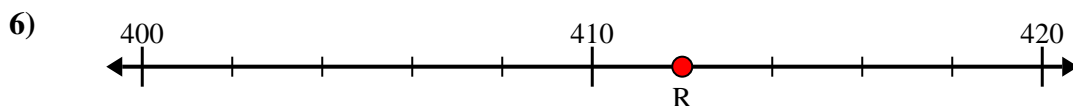


6. _____

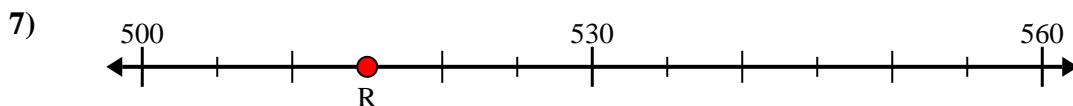


7. _____

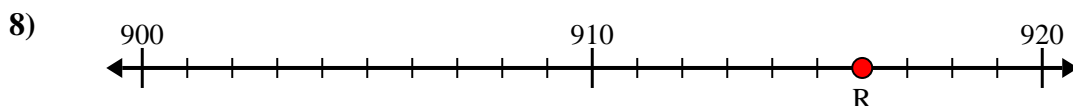

8. _____

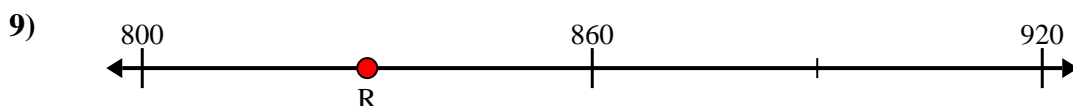











9. _____

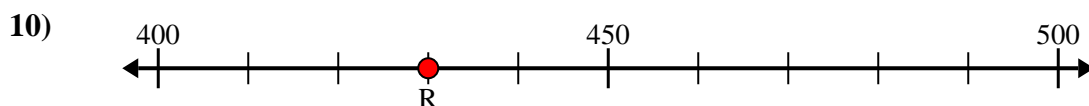

10. _____



Find the value of R.

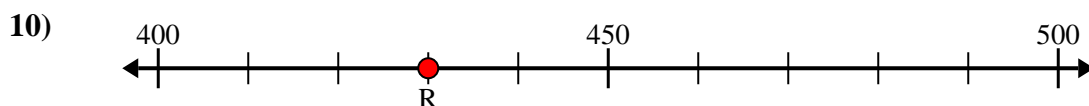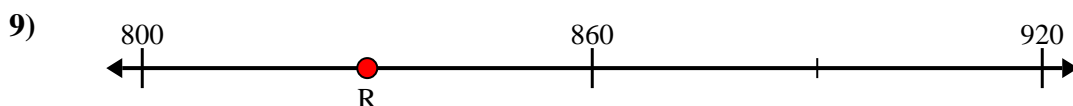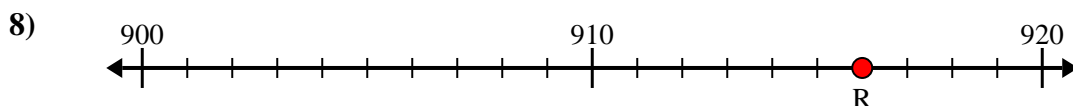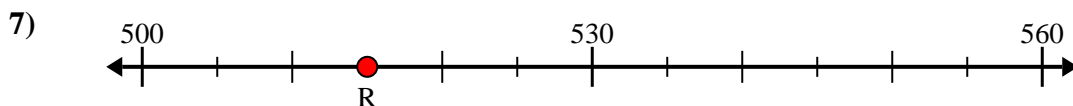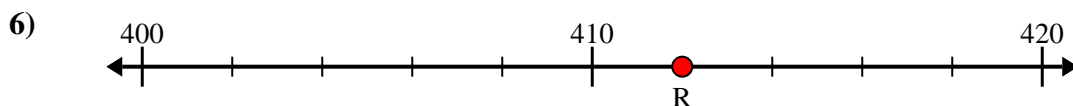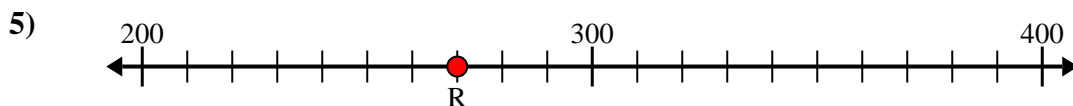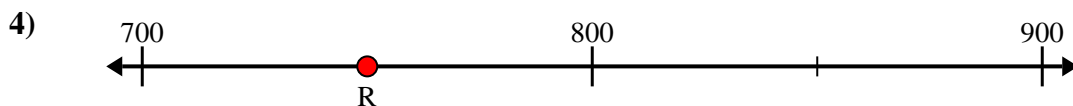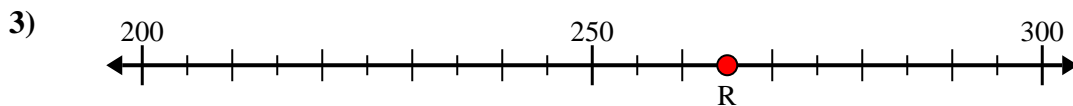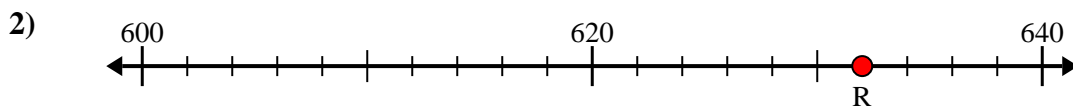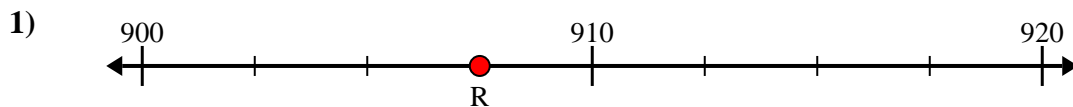

Answers

1. 907.5

2. 632

3. 265

4. 750

5. 270

6. 412

7. 515











8. 916

9. 830

10. 430



Find the value of R.

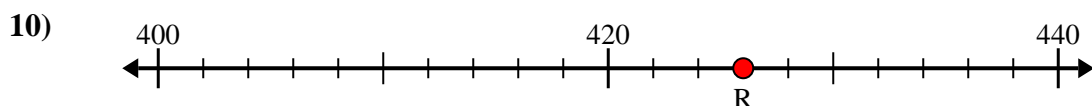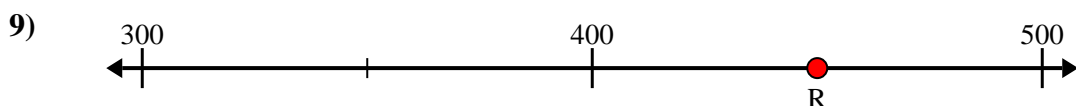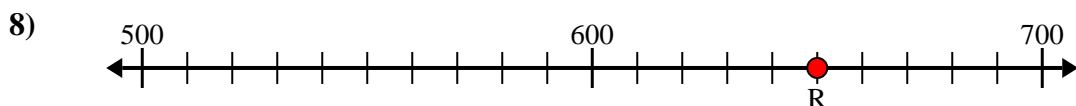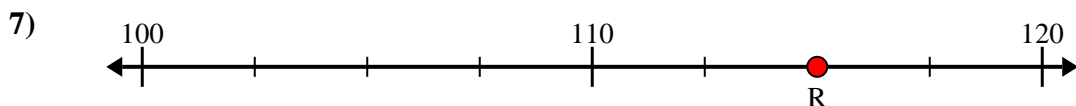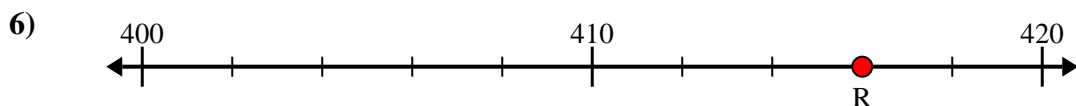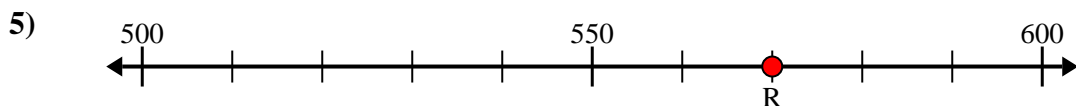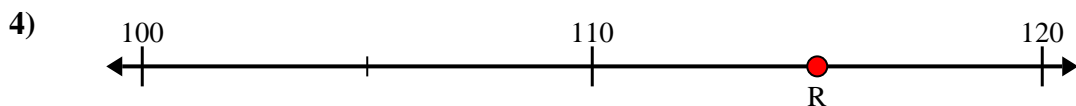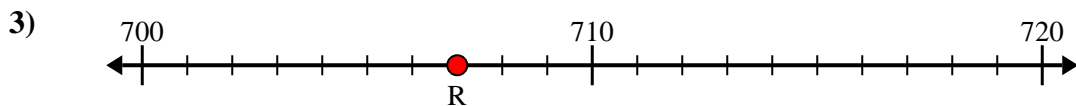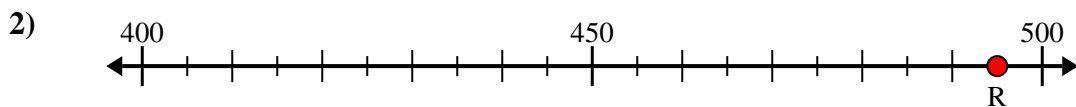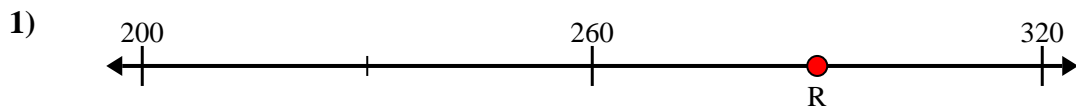

Answers

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Find the value of R.

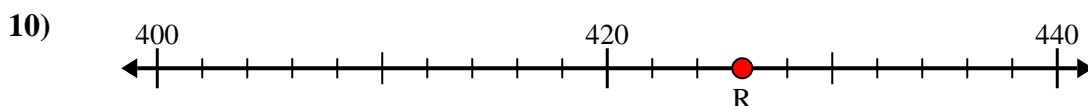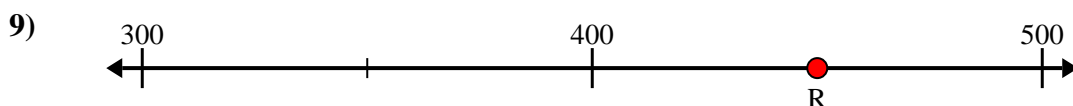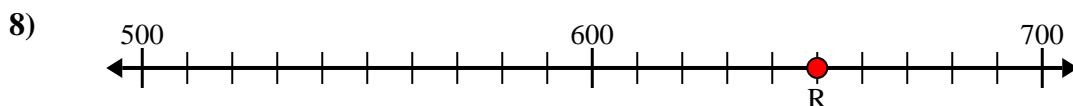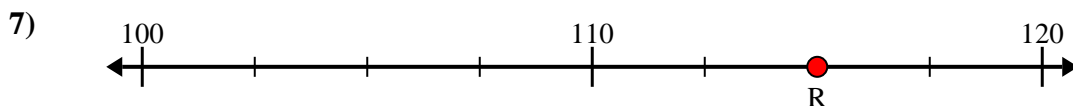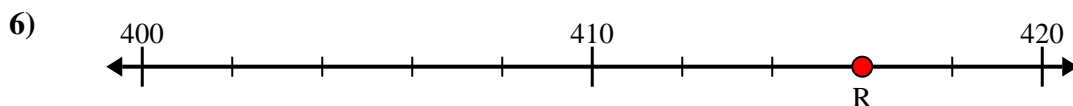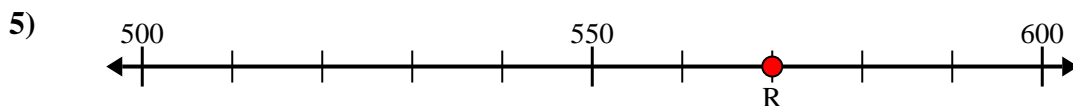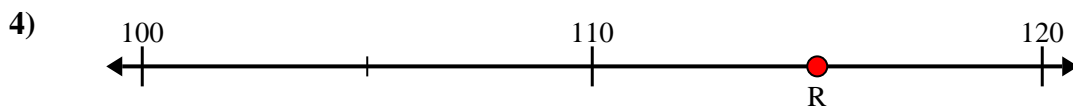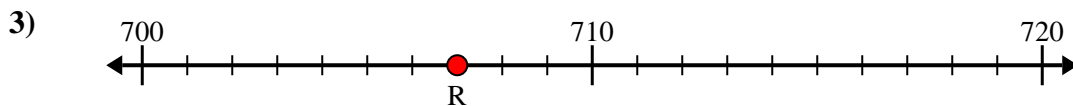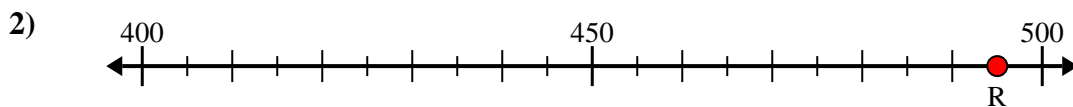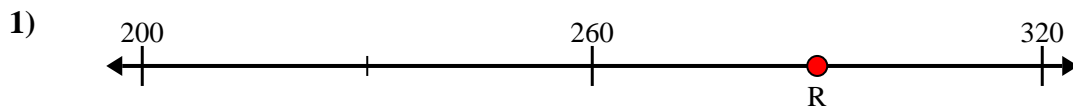

Answers

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650


9. 450

10. 426




Find the value of R.


Answers

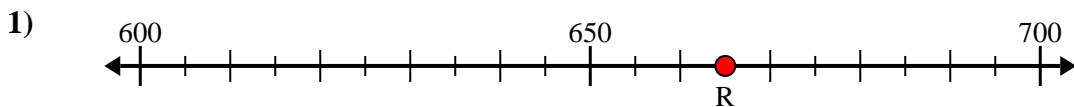


1. _____

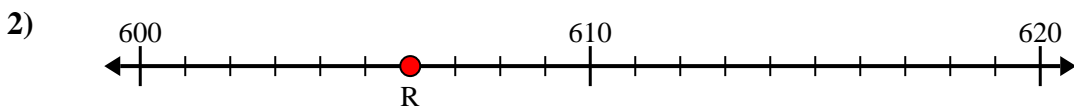


2. _____

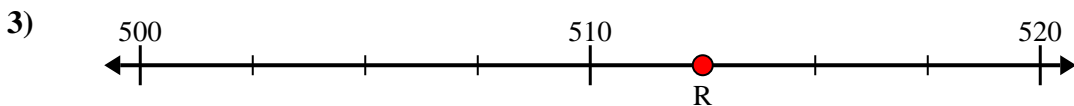


3. _____

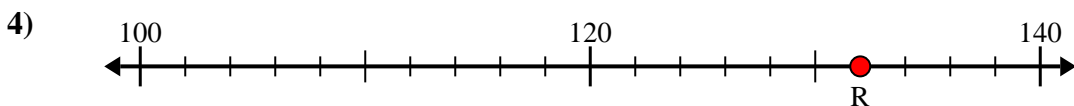


4. _____

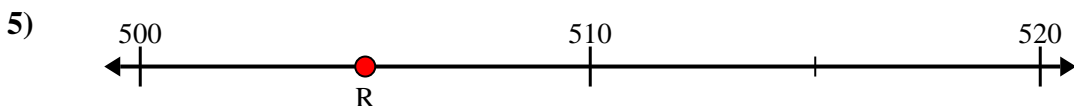


5. _____

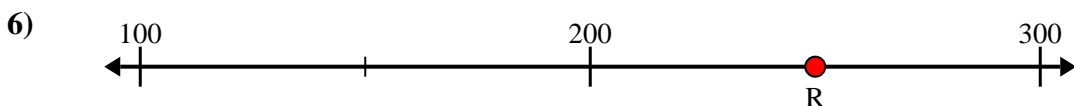


6. _____

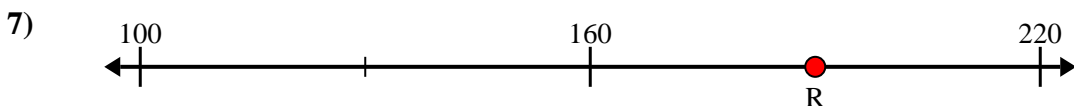


7. _____

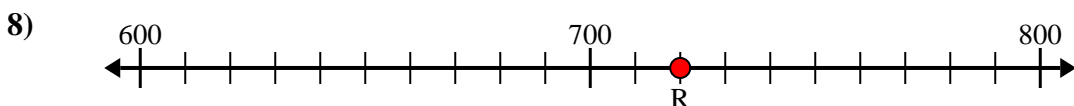

8. _____

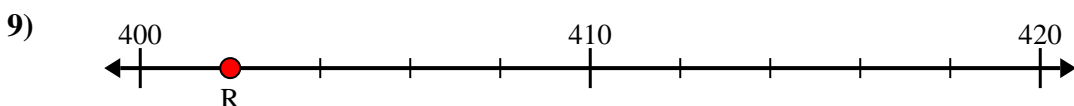











9. _____

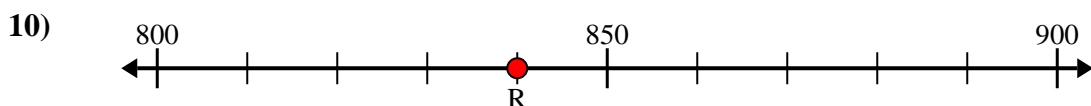

10. _____



Find the value of R.

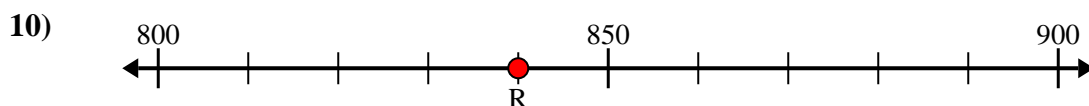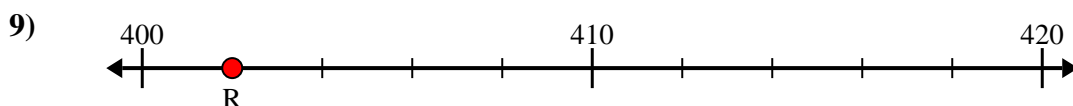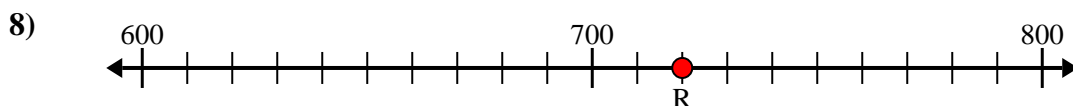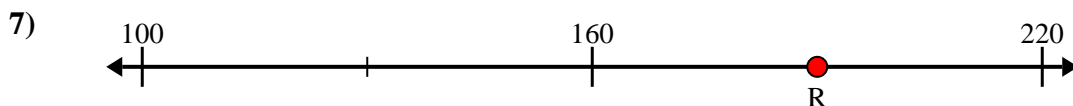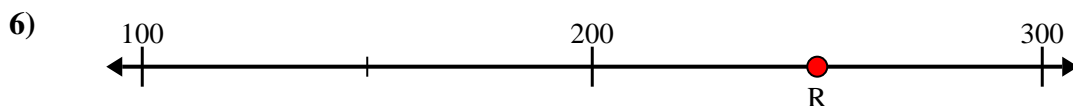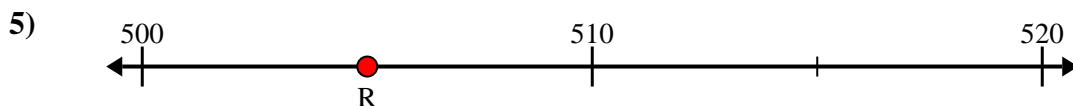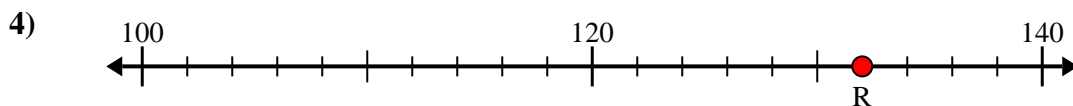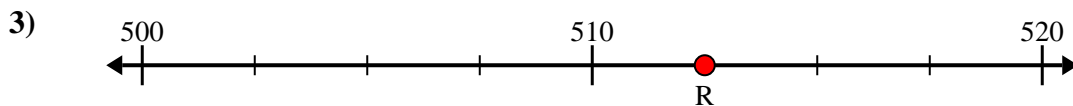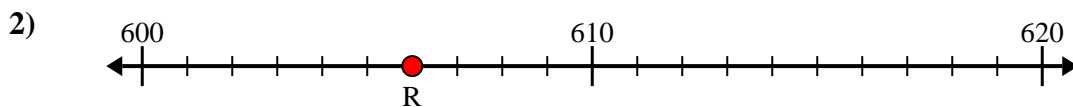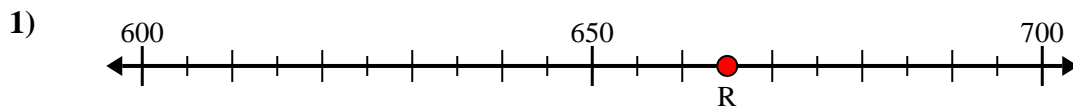

Answers

1. 665

2. 606

3. 512.5

4. 132

5. 505

6. 250

7. 190

8. 720


9. 402

10. 840




Find the value of R.


Answers

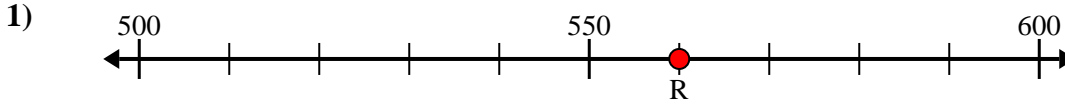


1. _____

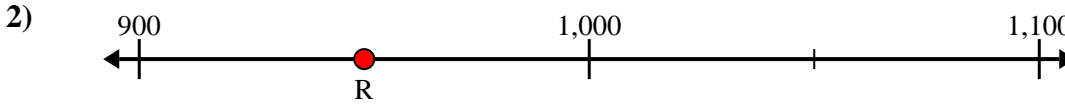


2. _____

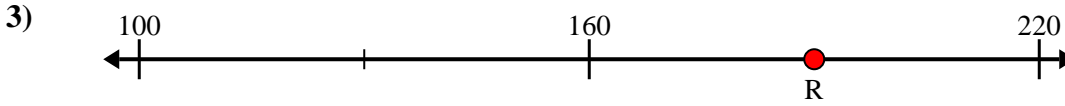


3. _____

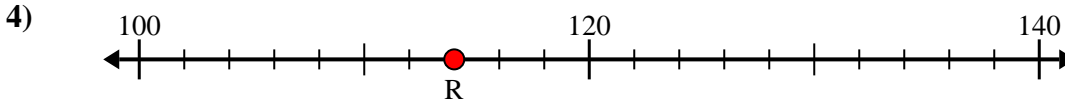


4. _____

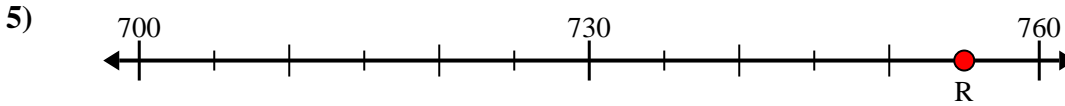


5. _____

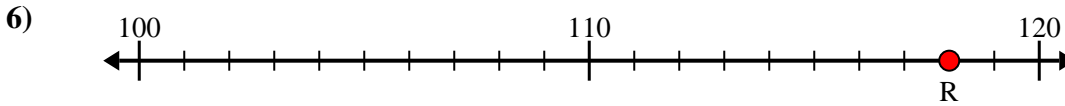


6. _____

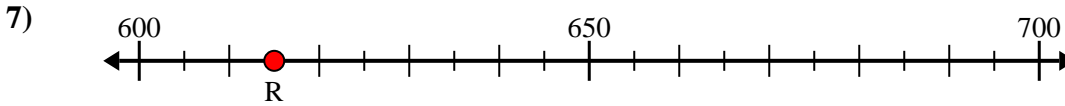


7. _____

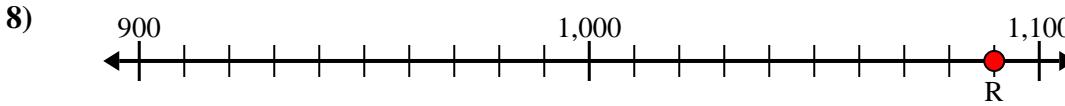

8. _____

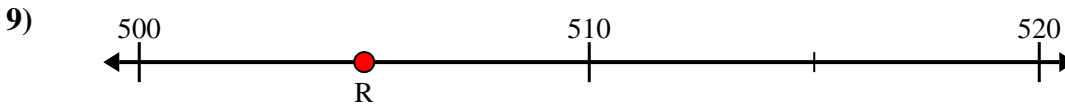











9. _____

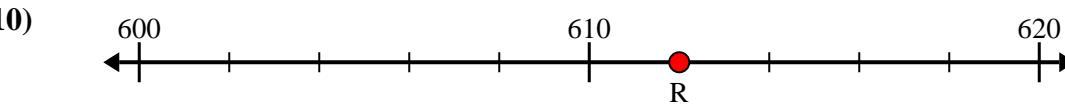

10. _____



Find the value of R.

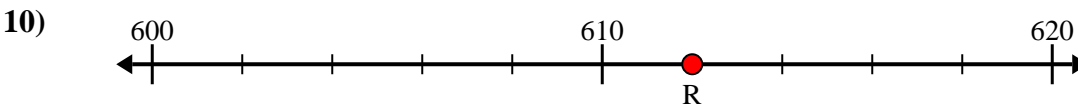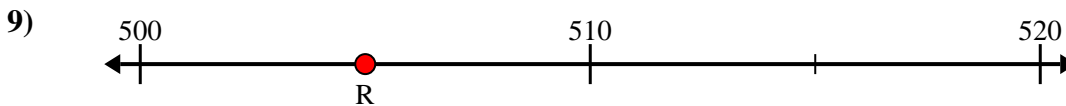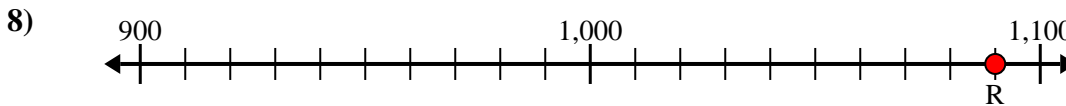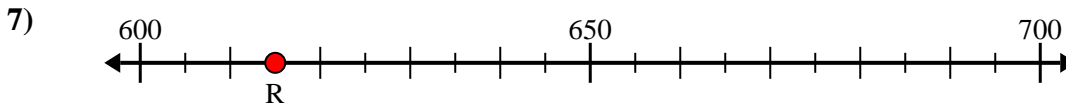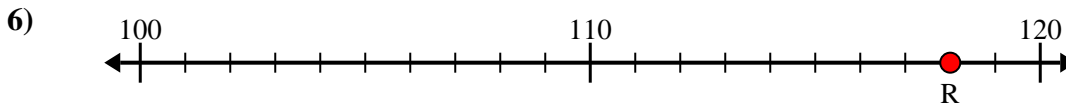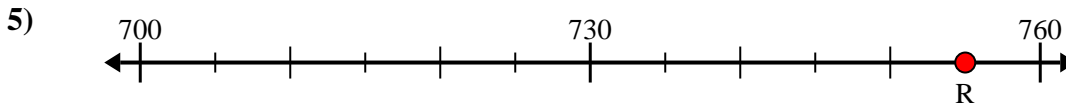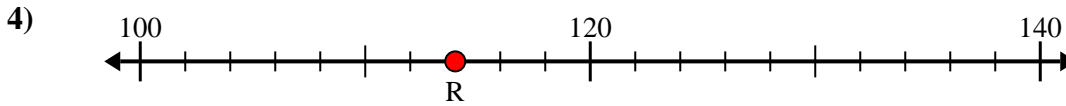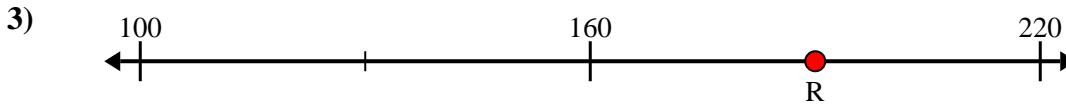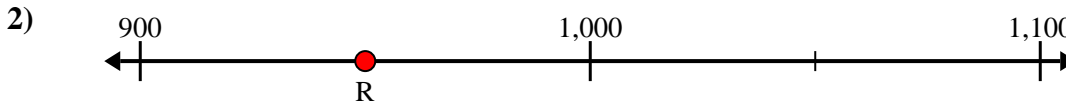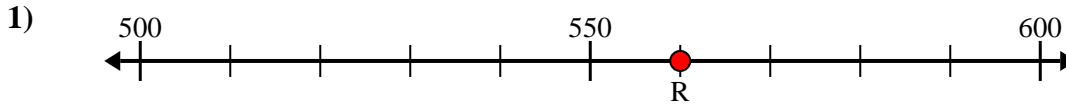

Answers

1. 560

2. 950

3. 190

4. 114

5. 755

6. 118

7. 615

8. 1,090


9. 505

10. 612




Find the value of R.


Answers

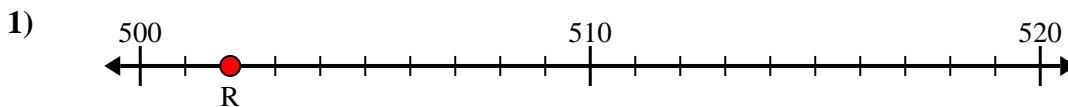


1. _____

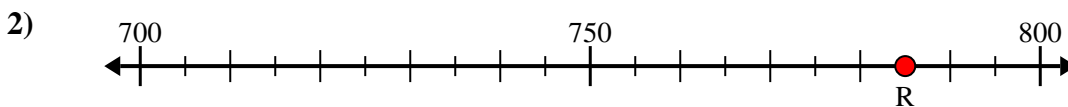


2. _____

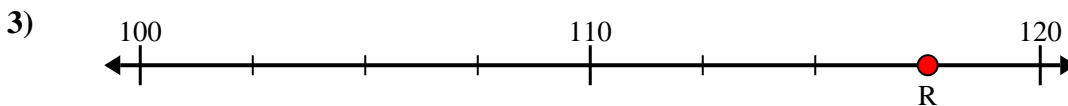


3. _____

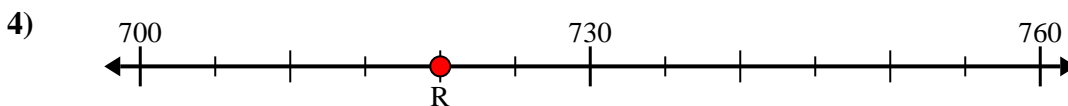


4. _____

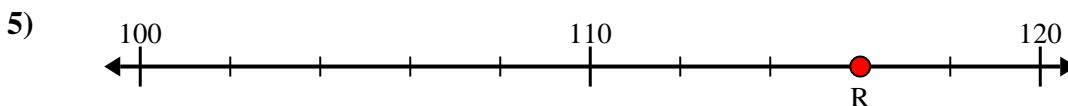


5. _____

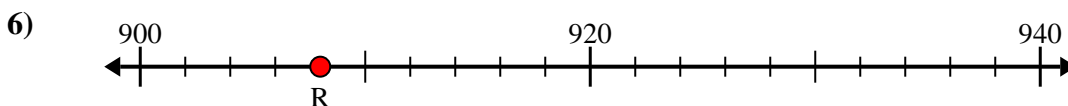


6. _____

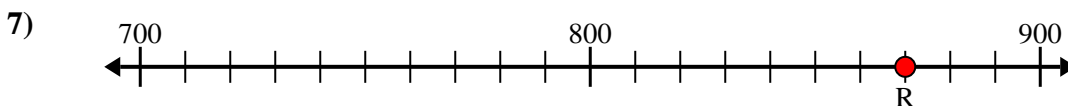


7. _____

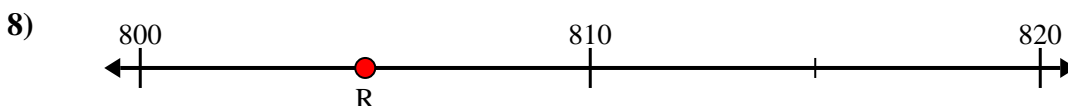

8. _____

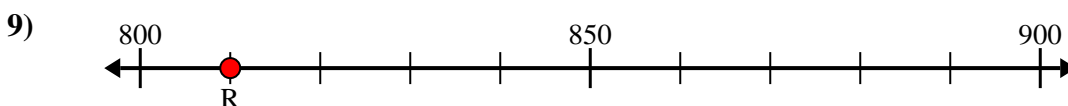











9. _____

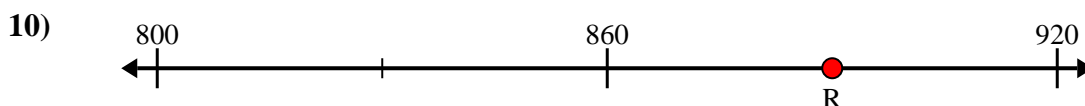

10. _____



Find the value of R.

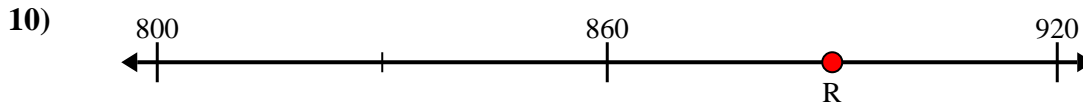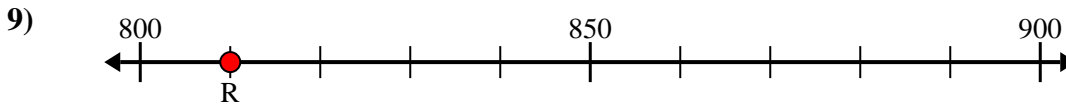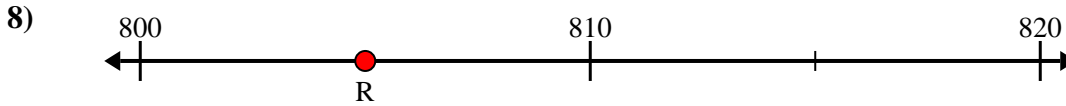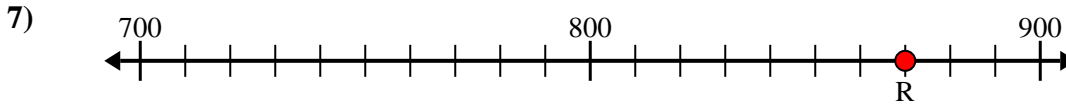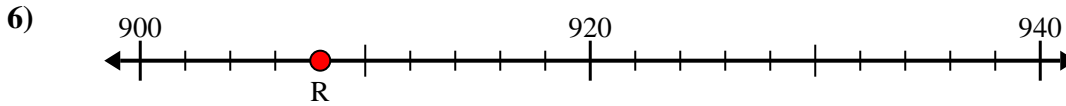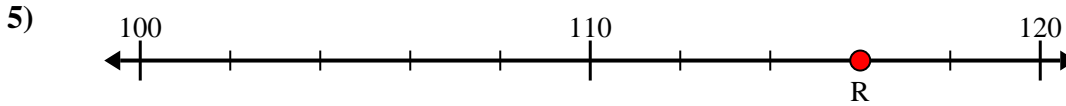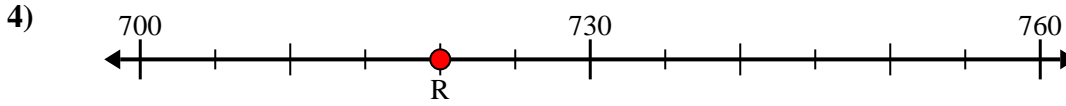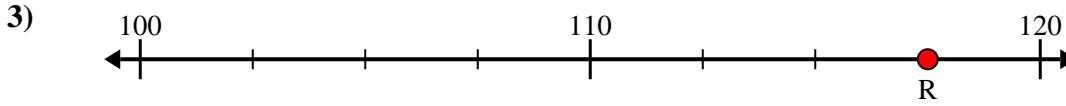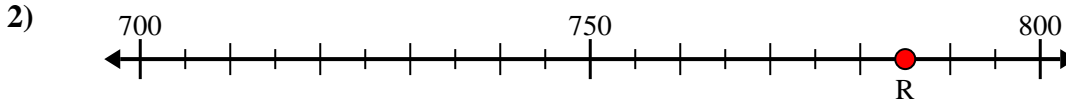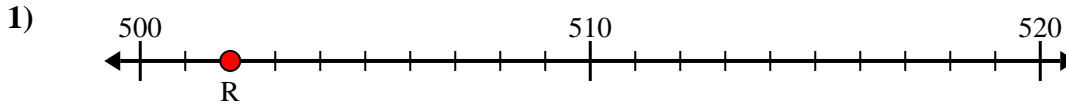

Answers

1. 502

2. 785

3. 117.5

4. 720

5. 116

6. 908

7. 870

8. 805


9. 810

10. 890




Find the value of R.


Answers

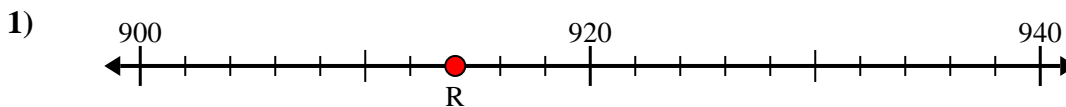


1. _____

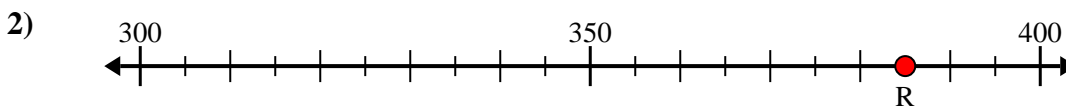


2. _____

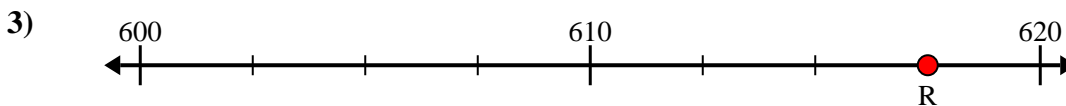


3. _____

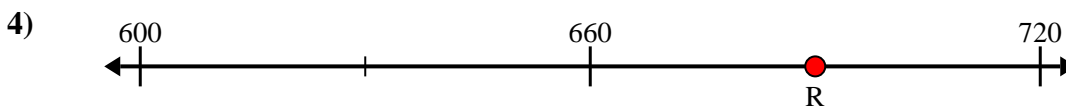


4. _____

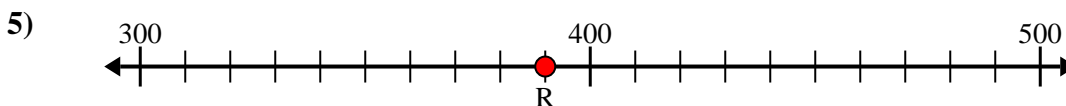


5. _____

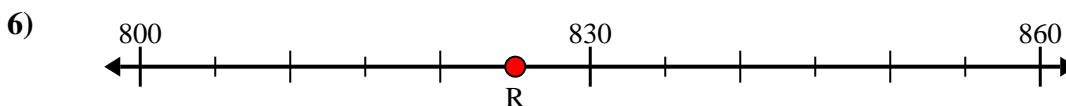


6. _____

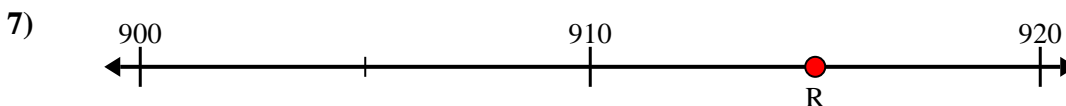


7. _____

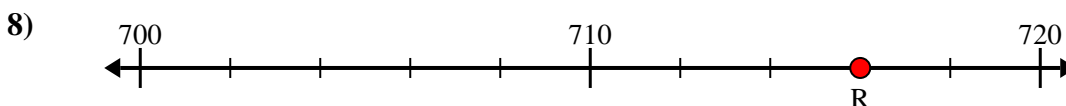

8. _____

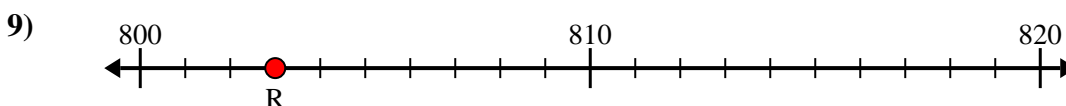











9. _____

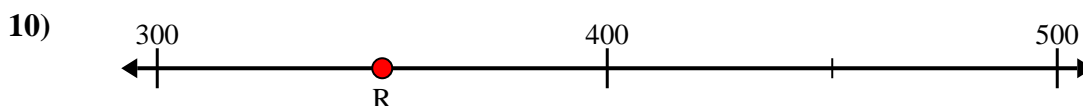

10. _____



Find the value of R.

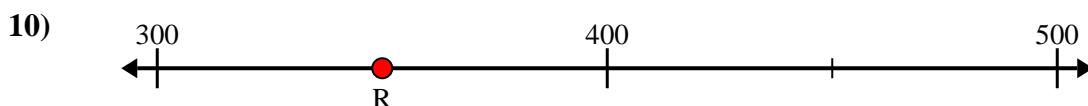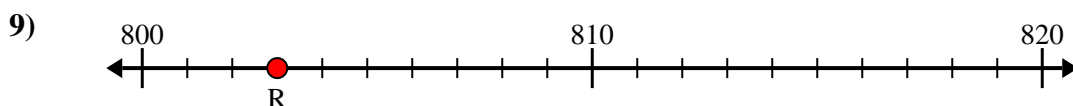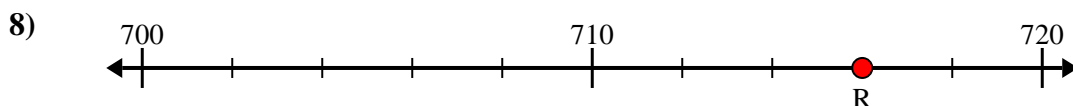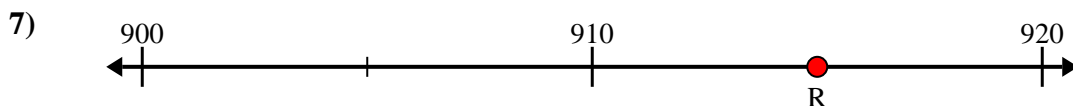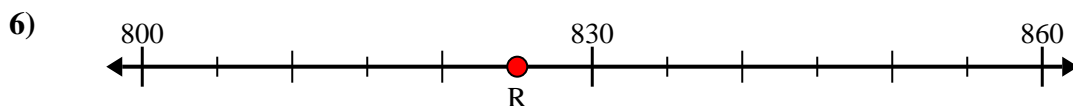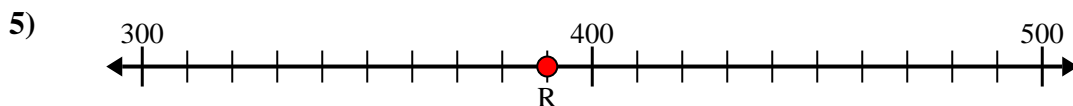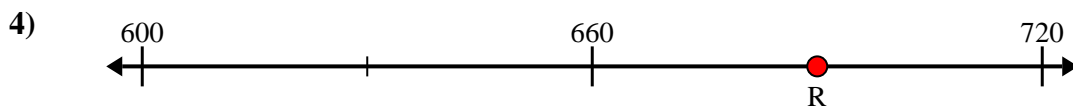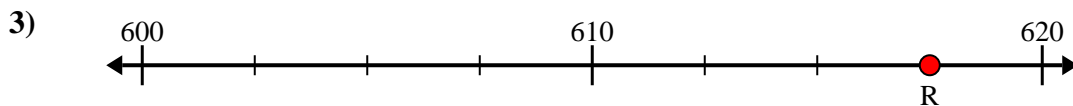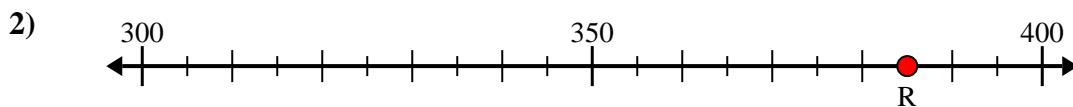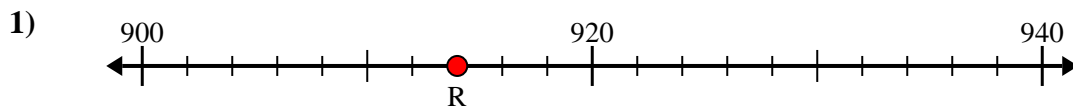

Answers

1. 914

2. 385

3. 617.5

4. 690

5. 390

6. 825

7. 915

8. 716


9. 803

10. 350




Find the value of R.


Answers

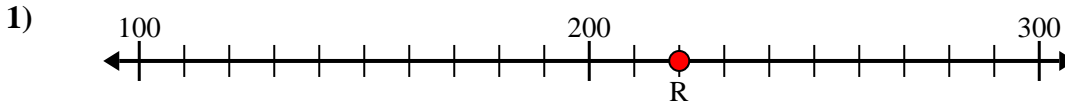


1. _____

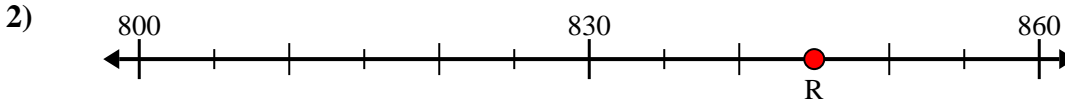


2. _____

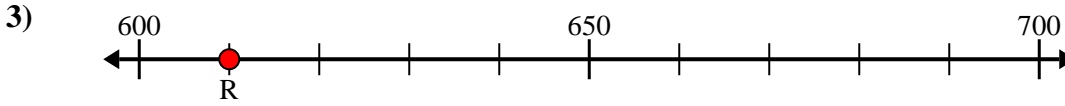


3. _____

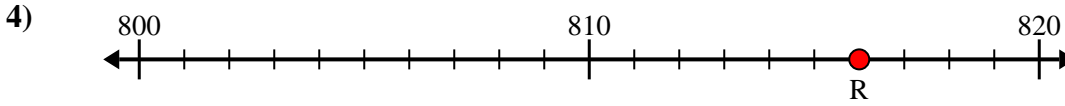


4. _____

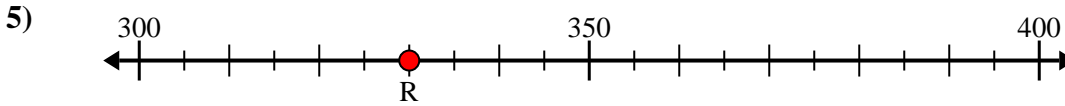


5. _____

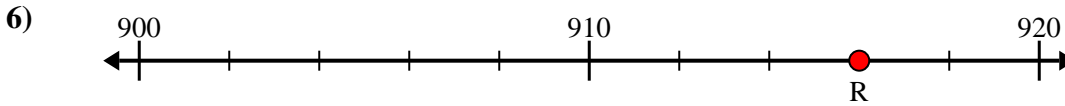


6. _____

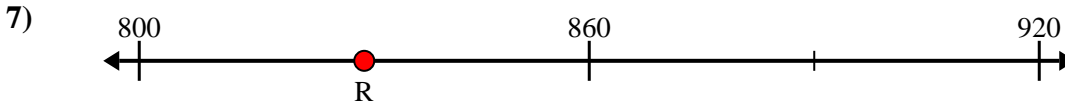


7. _____

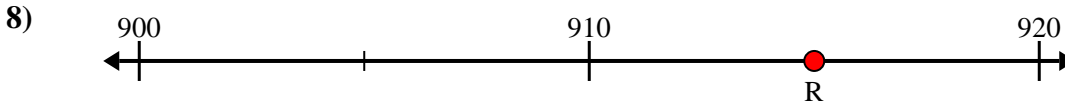

8. _____

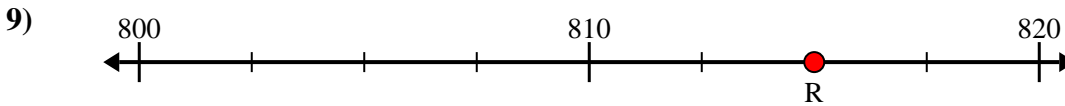











9. _____

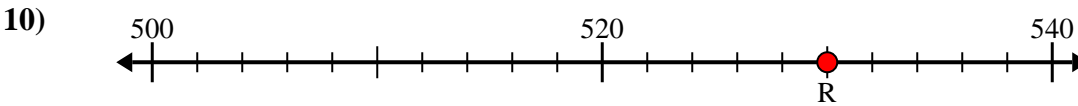

10. _____



Find the value of R.

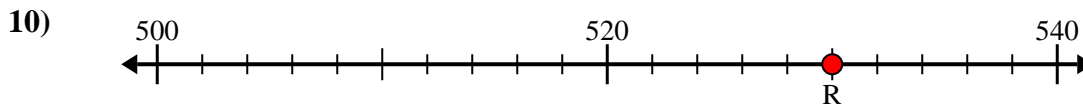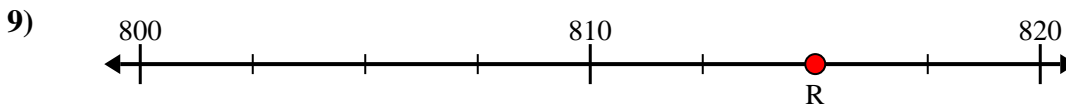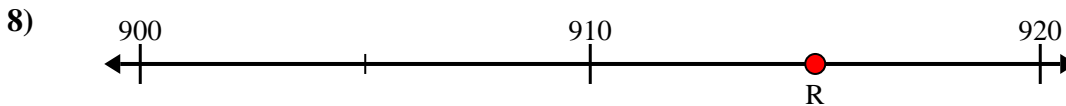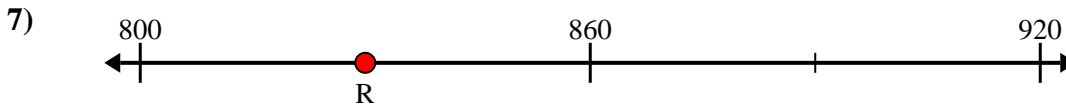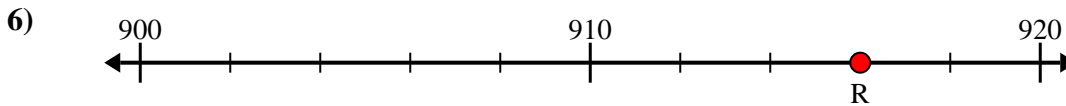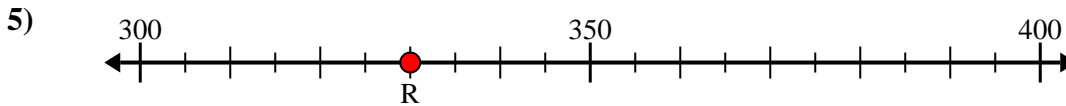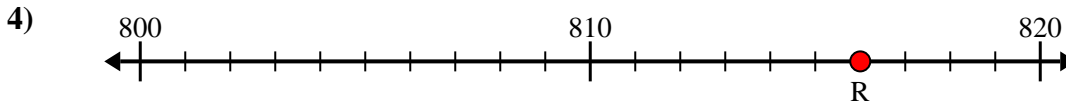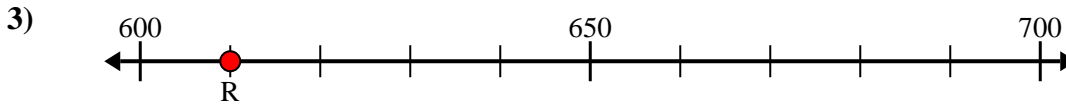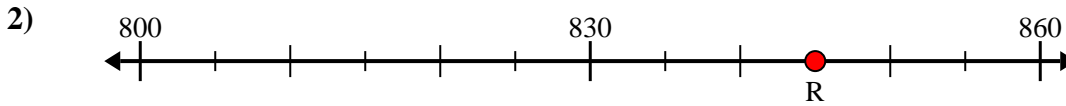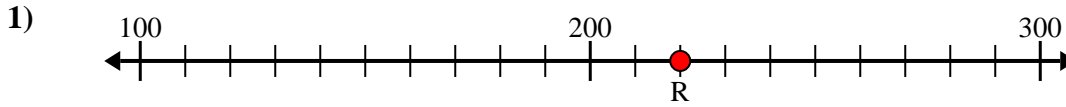

Answers

1. 220

2. 845

3. 610

4. 816

5. 330

6. 916

7. 830

8. 915


9. 815

10. 530




Find the value of R.


Answers

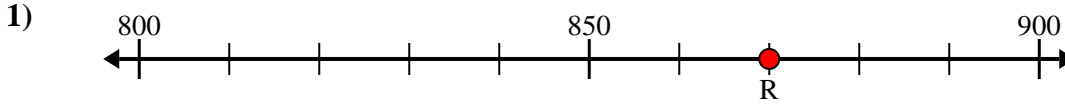


1. _____

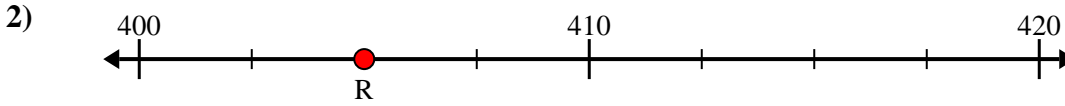


2. _____

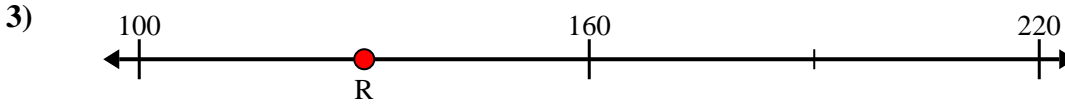


3. _____

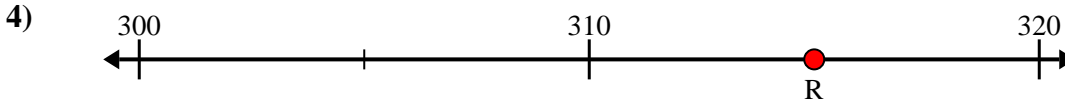


4. _____

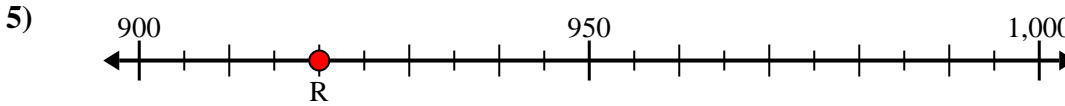


5. _____

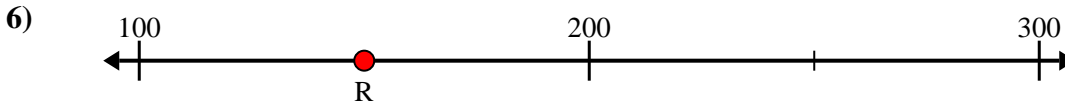


6. _____

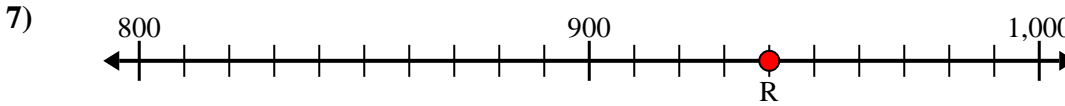


7. _____

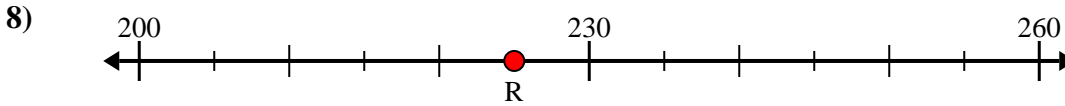

8. _____

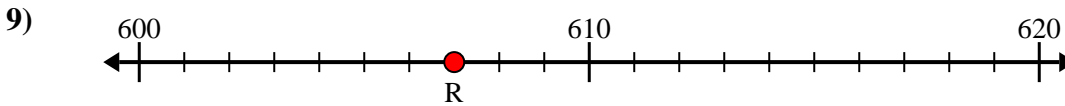











9. _____

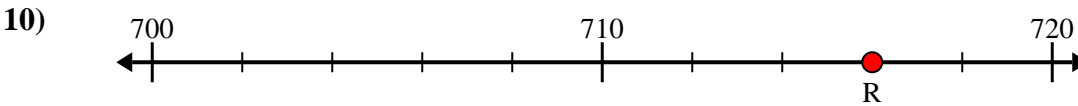

10. _____



Find the value of R.

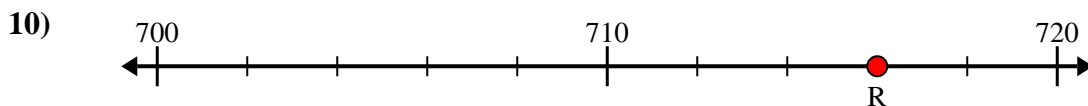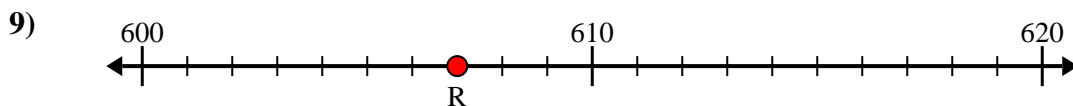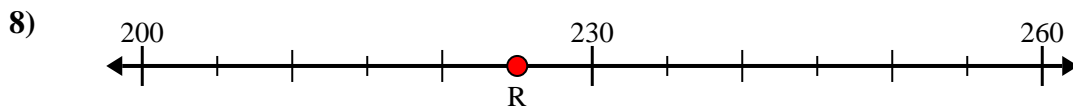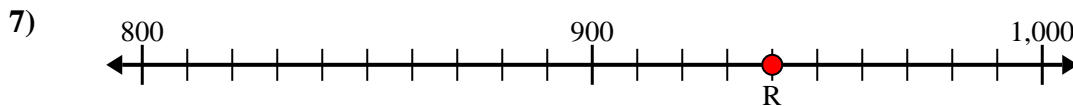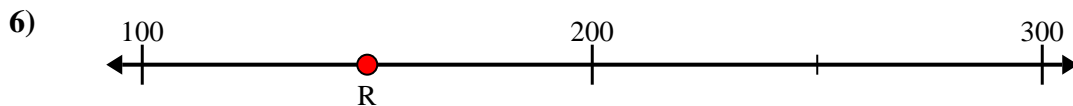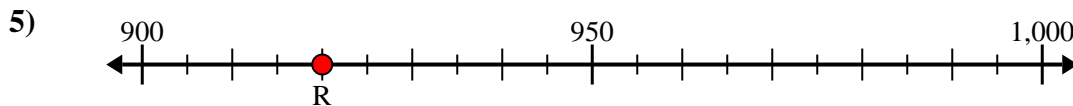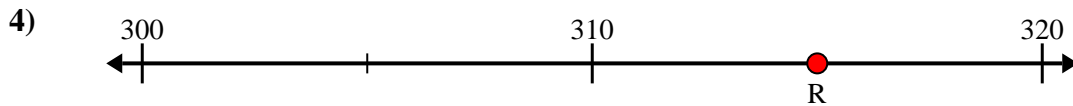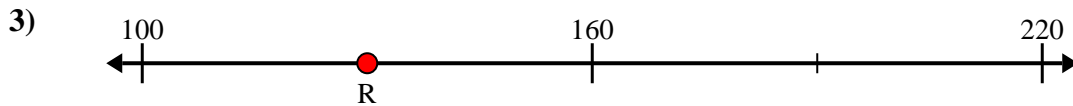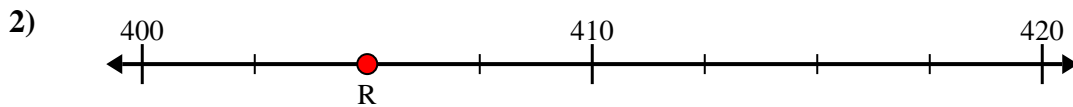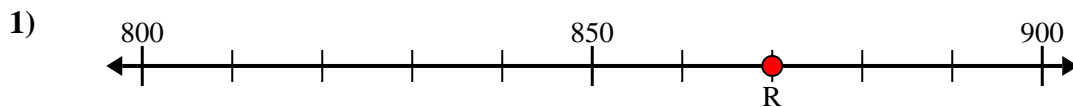

Answers

1. 870

2. 405

3. 130

4. 315

5. 920

6. 150

7. 940

8. 225

9. 607

10. 716