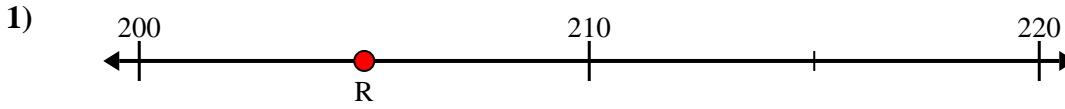





Find the value of R.


Answers




1. _____

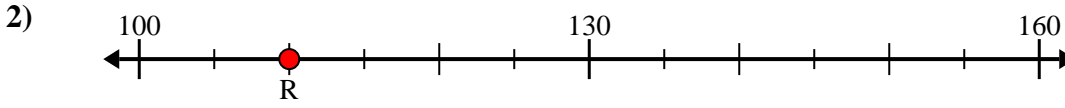


2. _____

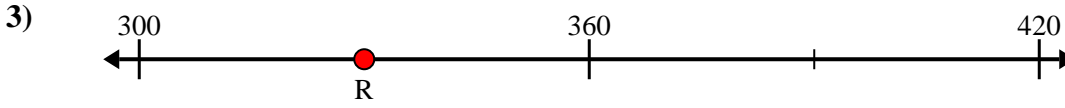


3. _____

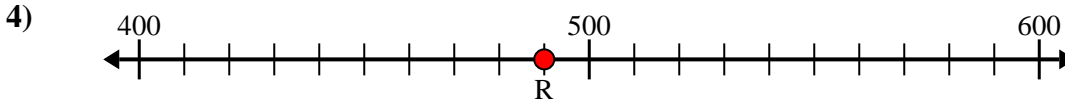


4. _____

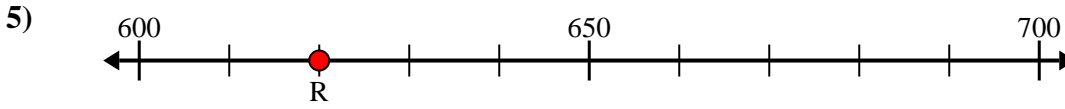


5. _____

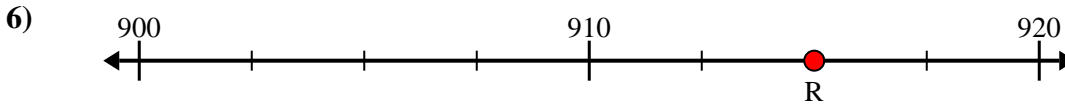


6. _____

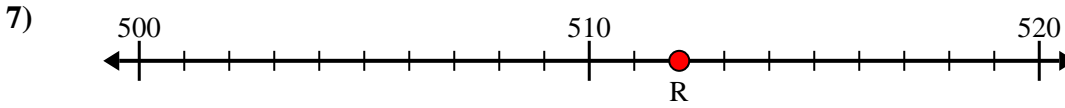


7. _____

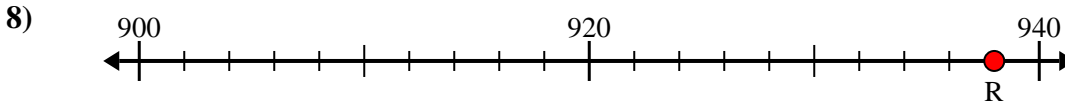

8. _____

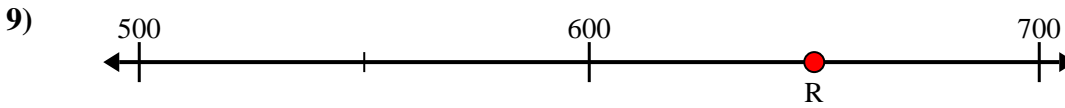











9. _____

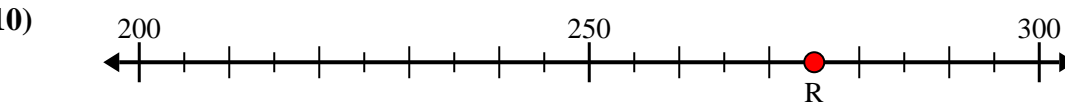

10. _____



Find the value of R.

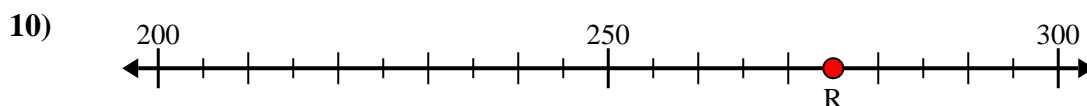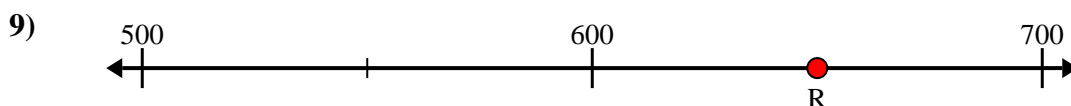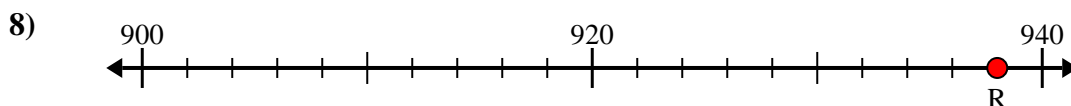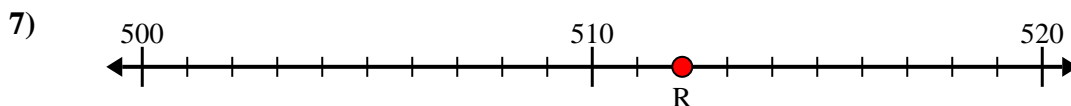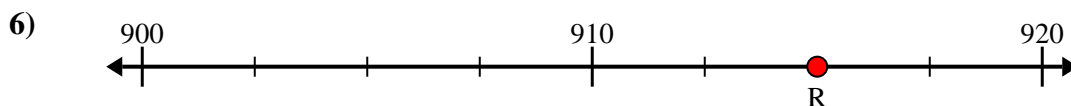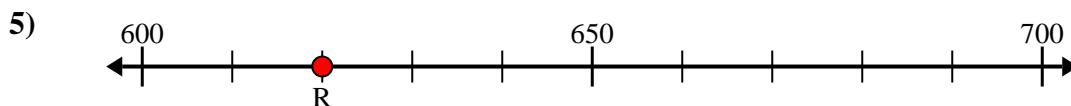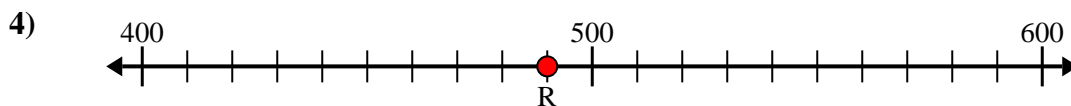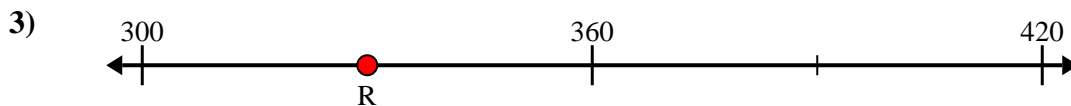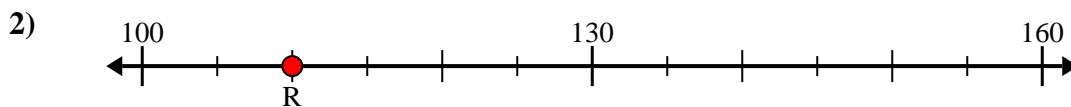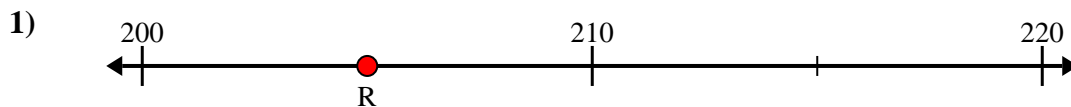**Answers**1. 2052. 1103. 3304. 4905. 6206. 9157. 5128. 9389. 65010. 275