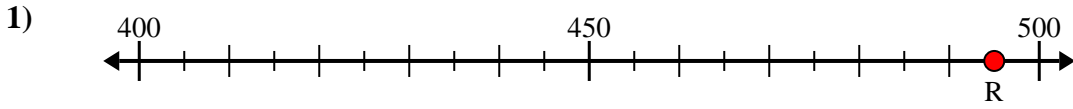





Find the value of R.


Answers




1. _____

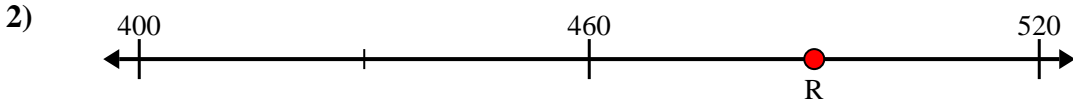


2. _____

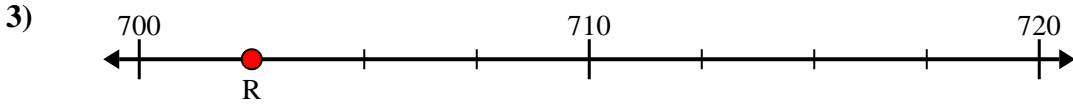


3. _____

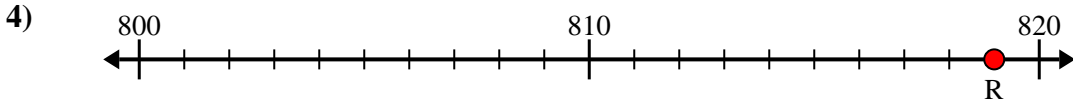


4. _____

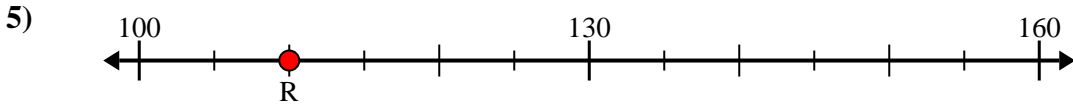


5. _____

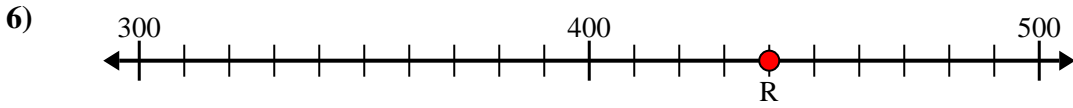


6. _____

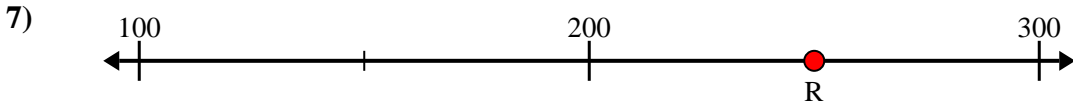


7. _____

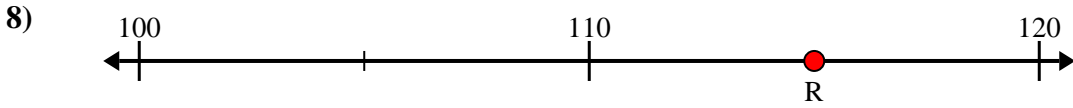

8. _____

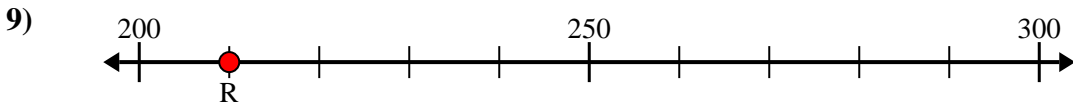











9. _____

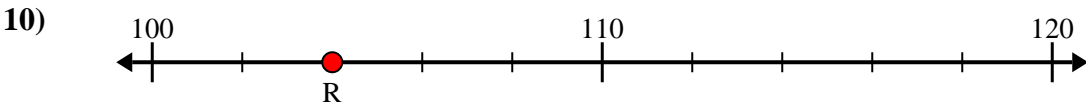

10. _____



Find the value of R.

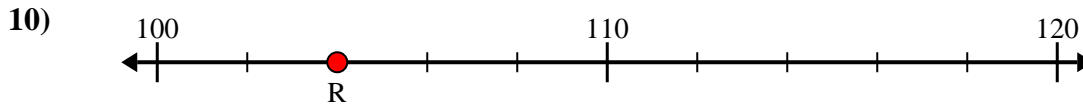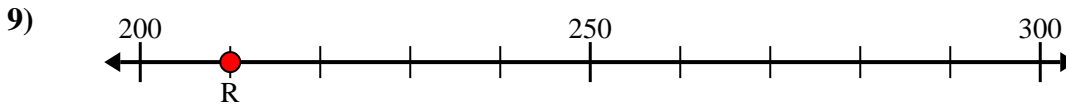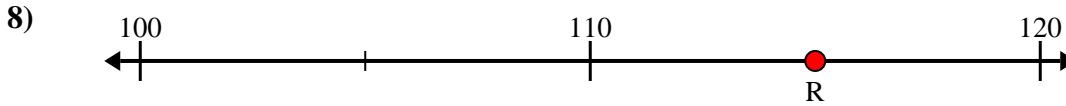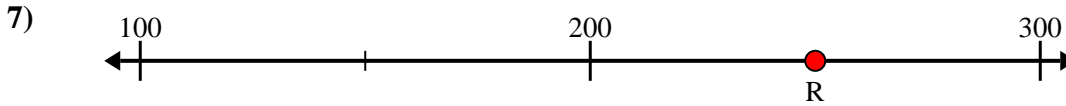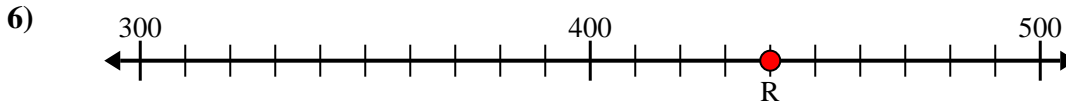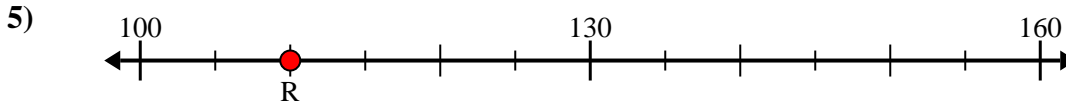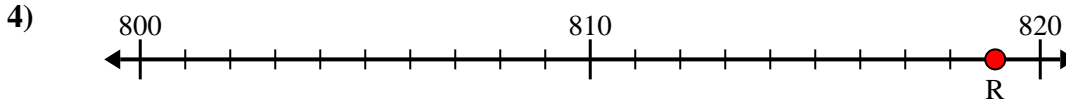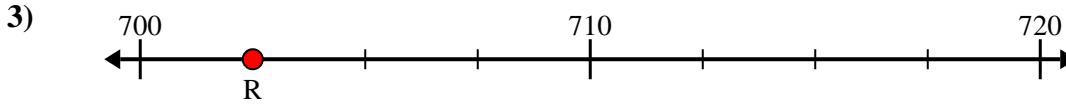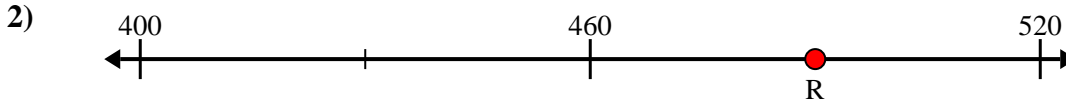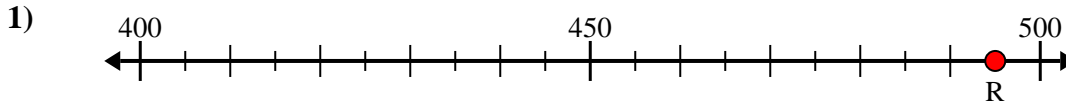

Answers

1. 495

2. 490

3. 702.5

4. 819

5. 110

6. 440

7. 250

8. 115

9. 210

10. 104