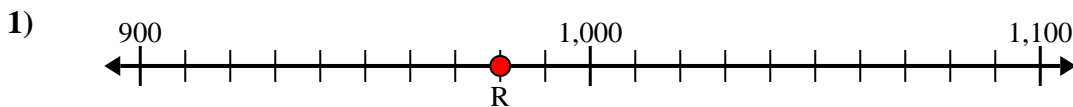





Find the value of R.


Answers




1. _____

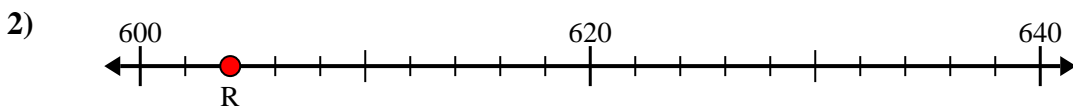


2. _____

 


3. _____

 


4. _____

 


5. _____

 


6. _____

 


7. _____

 

8. _____

 











9. _____

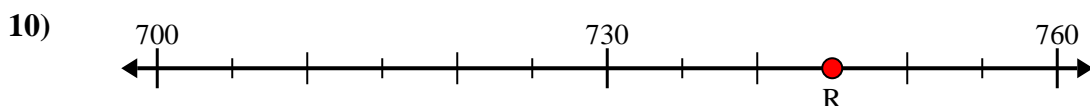

10. _____



Find the value of R.

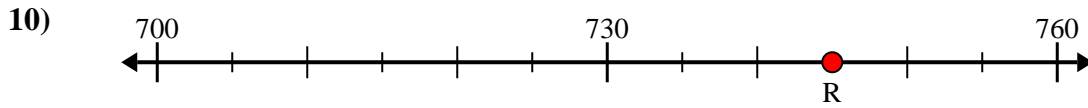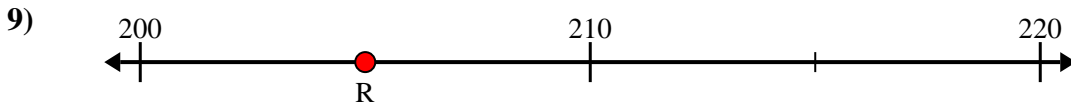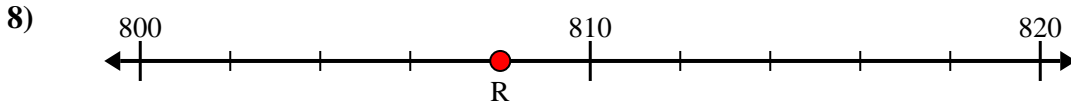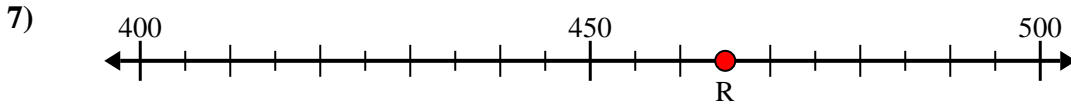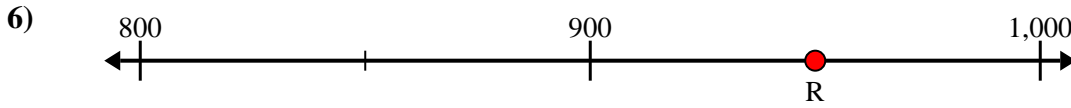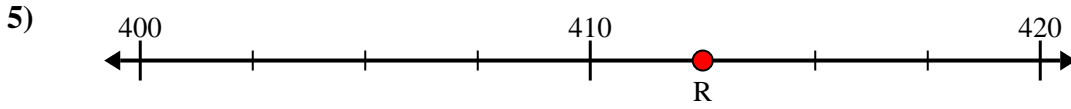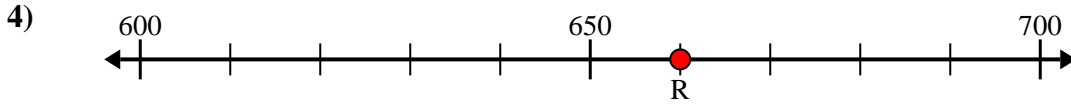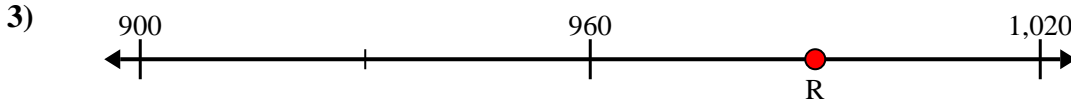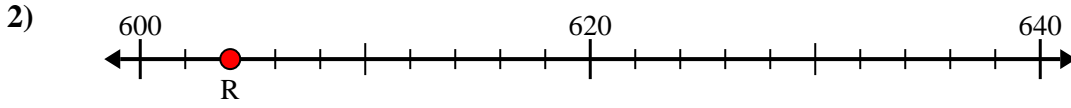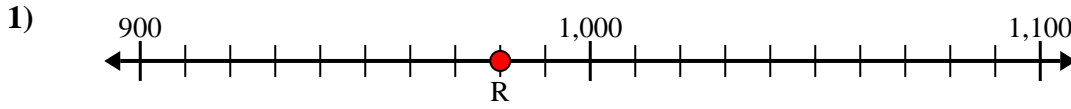

Answers

1. 980

2. 604

3. 990

4. 660

5. 412.5

6. 950

7. 465

8. 808

9. 205

10. 745