

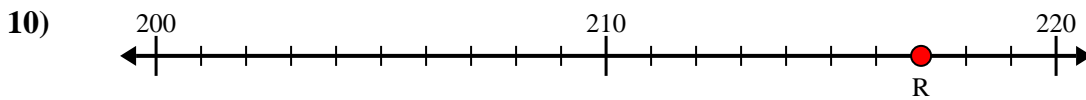
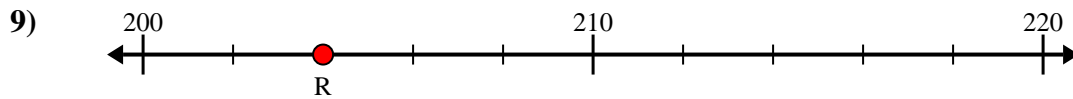
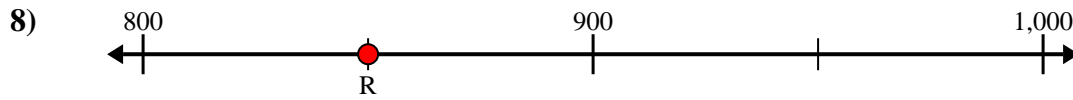
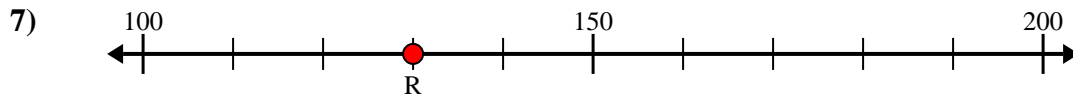
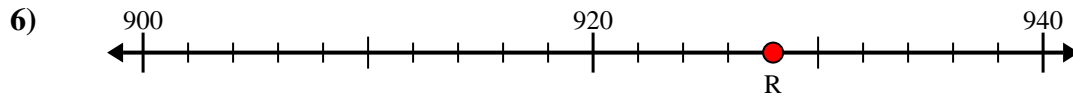
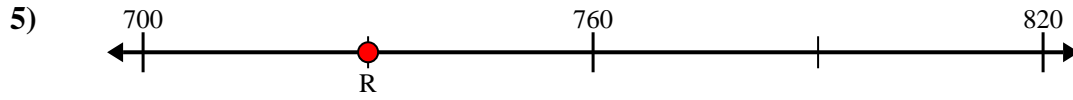
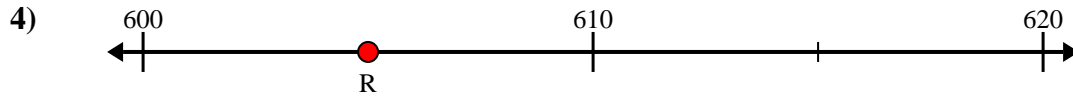
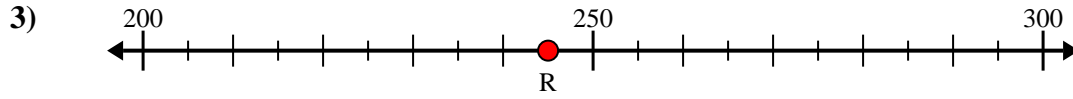


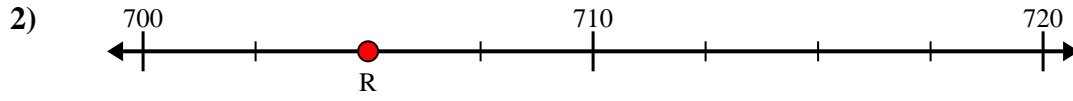

Find the value of R.










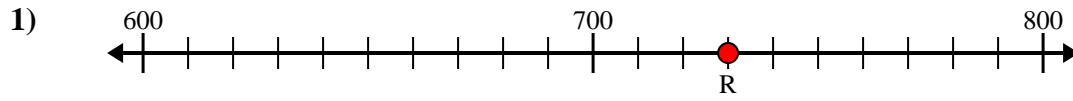


Answers

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Find the value of R.

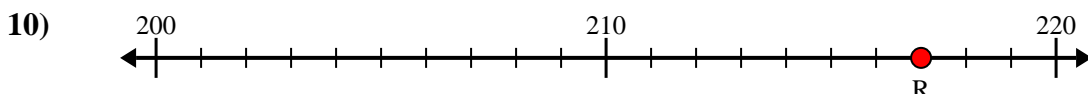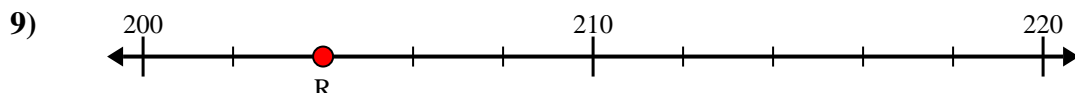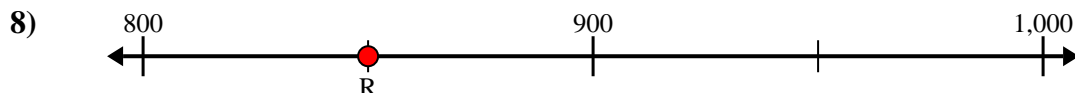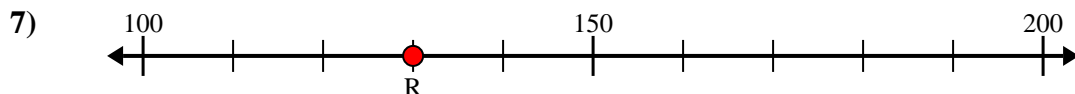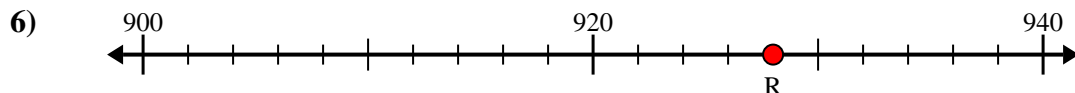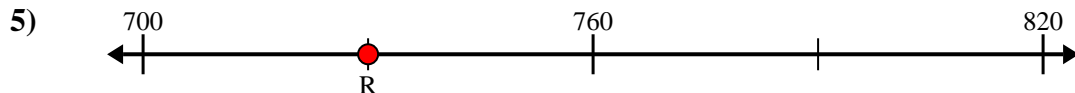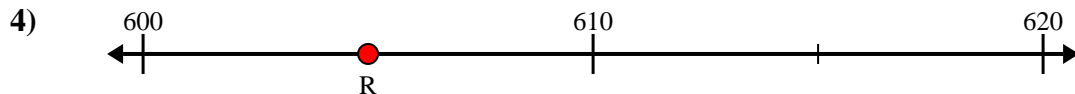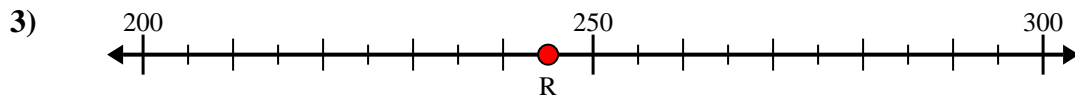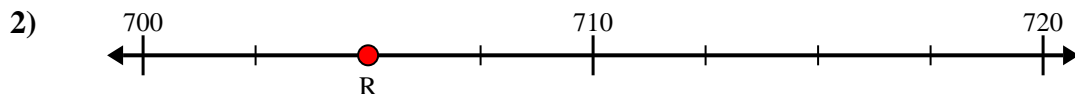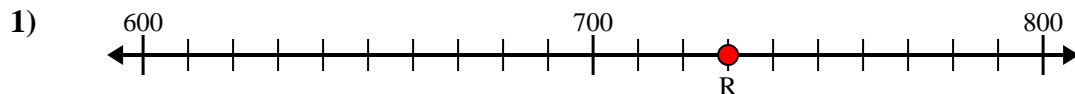

Answers

1. 730
2. 705
3. 245
4. 605
5. 730
6. 928
7. 130
8. 850
9. 204
10. 217