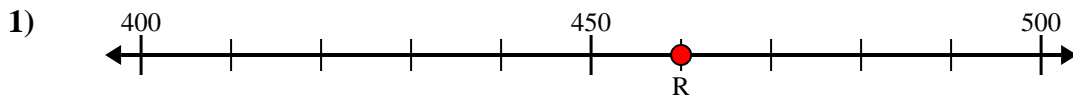





Find the value of R.


Answers




1. _____

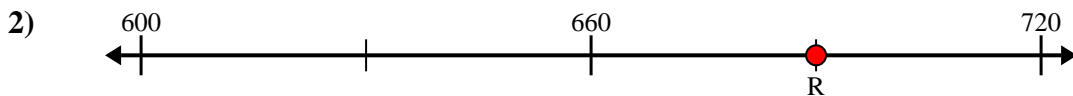


2. _____

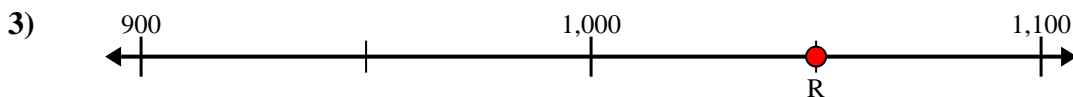


3. _____

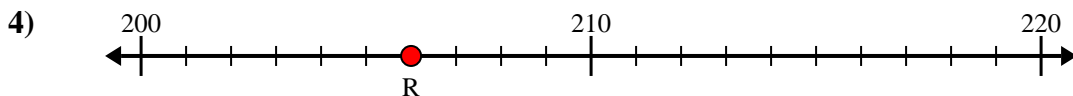


4. _____

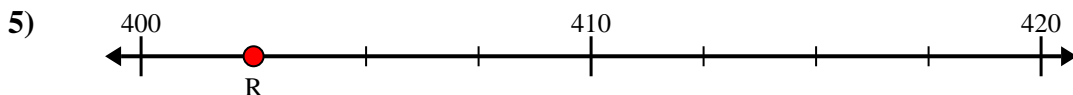


5. _____

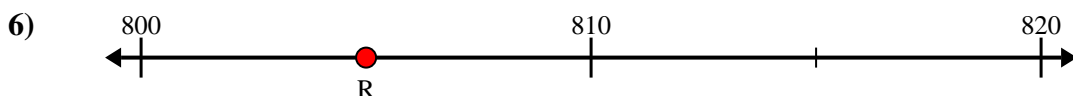


6. _____

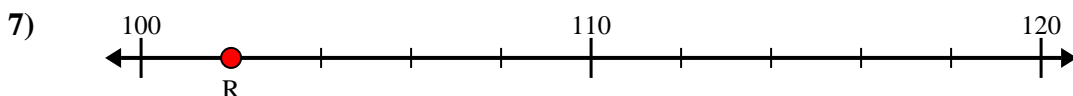


7. _____

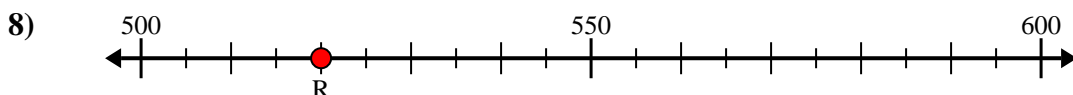

8. _____

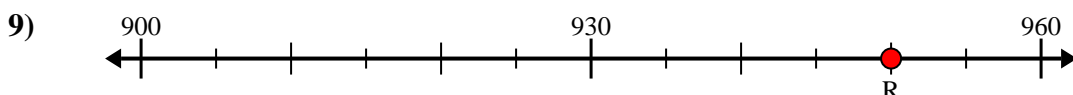











9. _____

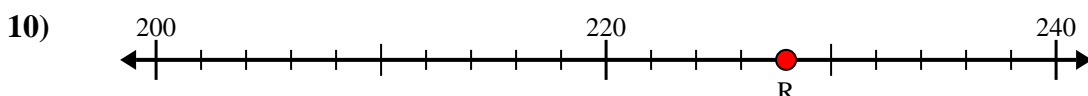

10. _____



Find the value of R.

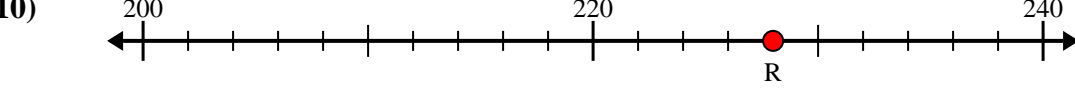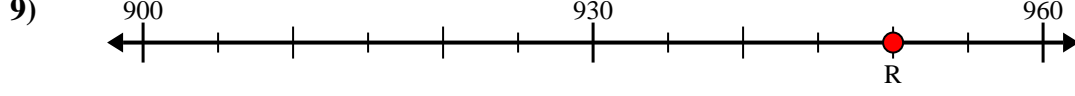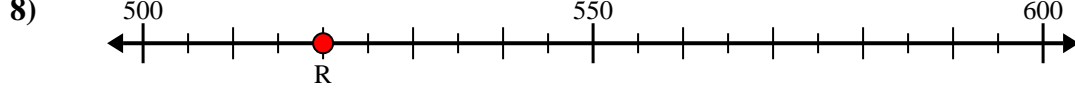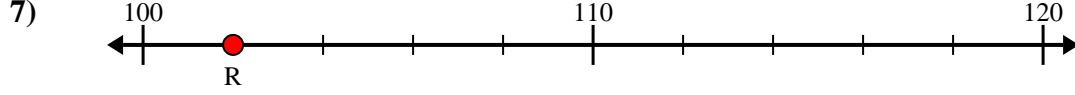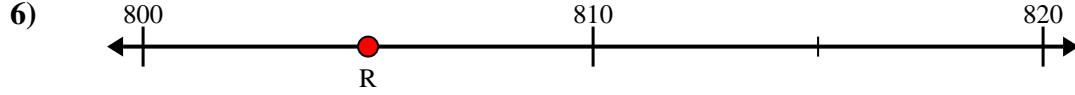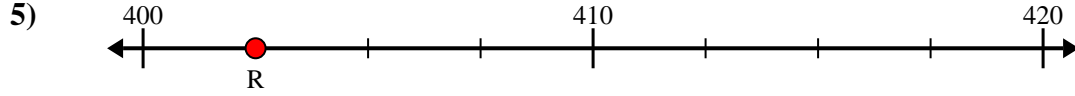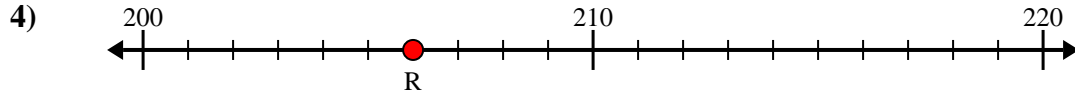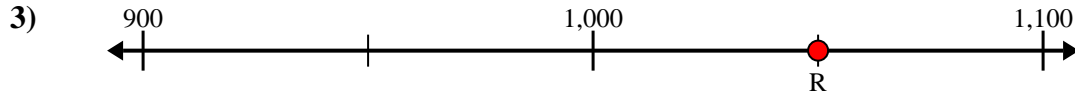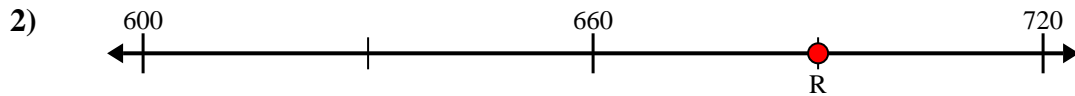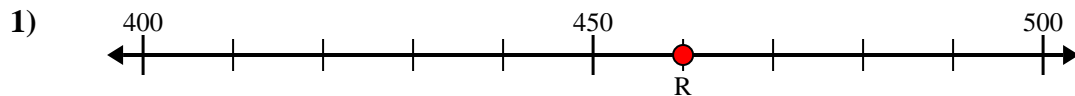

Answers

1. 460
2. 690
3. 1,050
4. 206
5. 403
6. 805
7. 102
8. 520
9. 950
10. 228