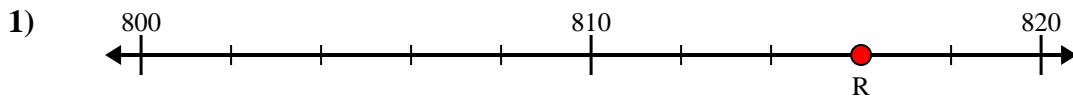





Find the value of R.


Answers




1. _____

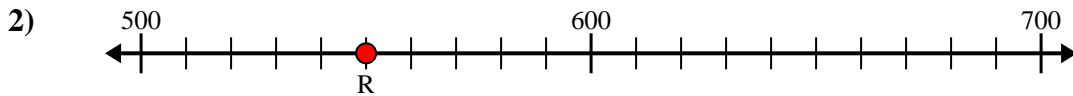


2. _____

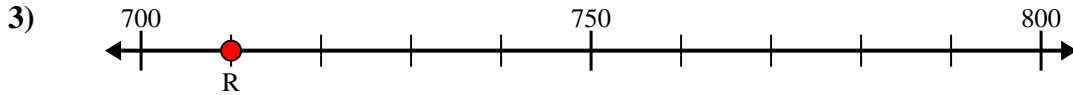


3. _____

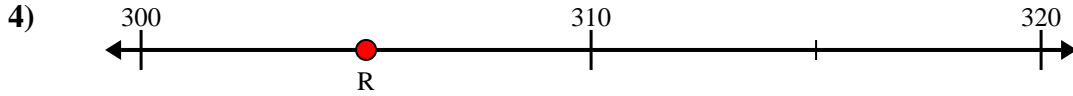


4. _____

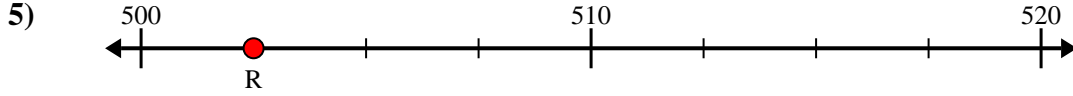


5. _____

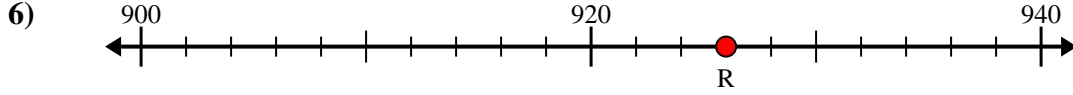


6. _____

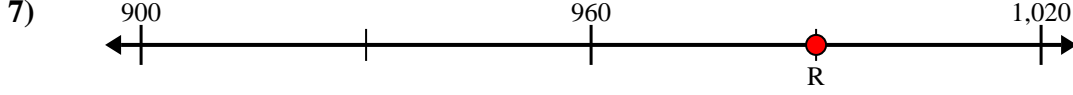


7. _____

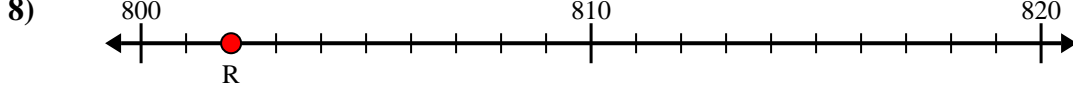

8. _____

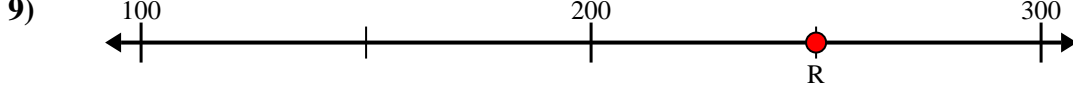











9. _____

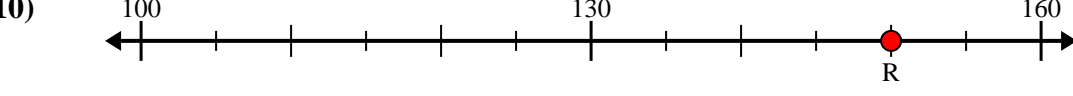

10. _____



Find the value of R.

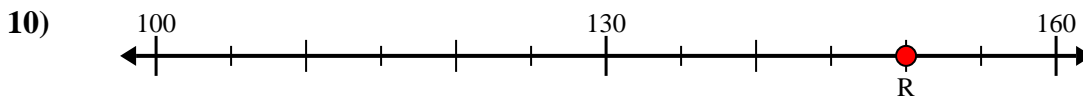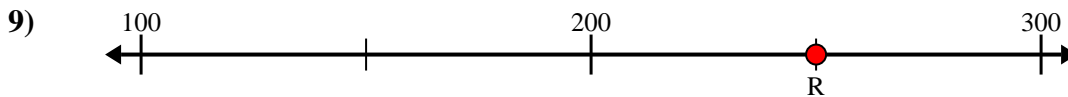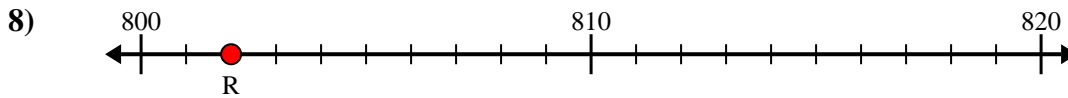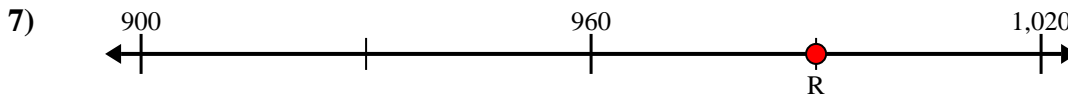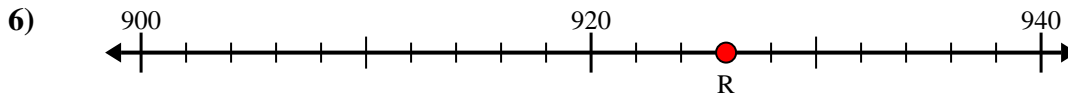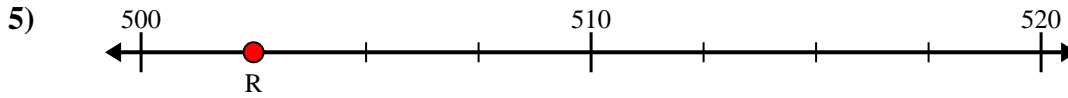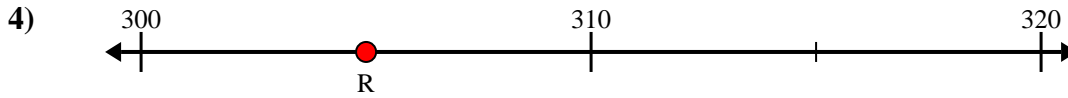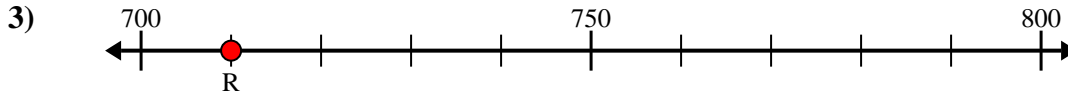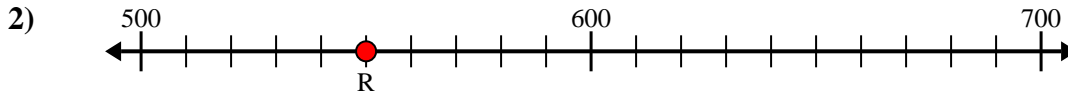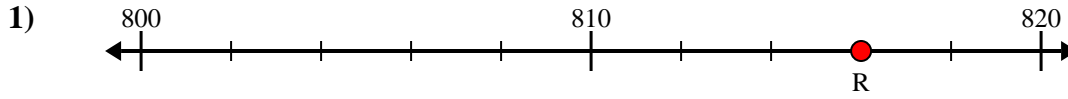

Answers

1. 816

2. 550

3. 710

4. 305

5. 503

6. 926

7. 990

8. 802

9. 250

10. 150