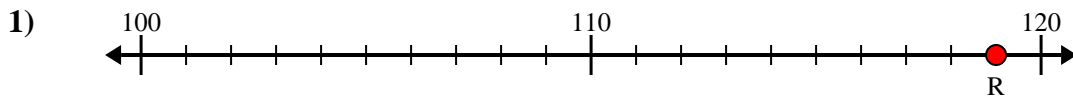





Find the value of R.


Answers




1. _____

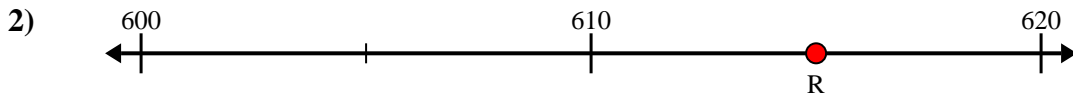


2. _____

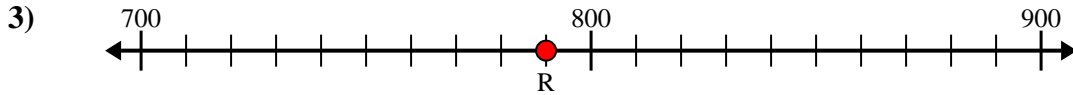


3. _____

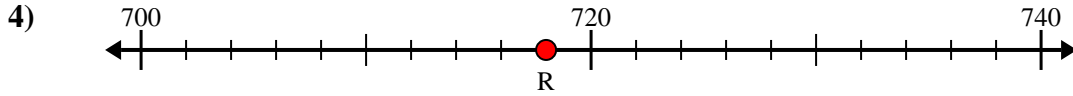


4. _____

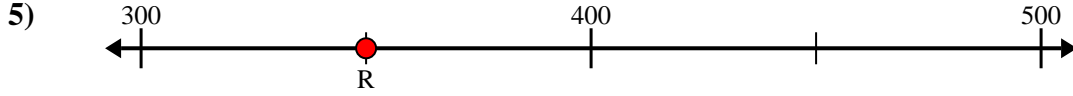


5. _____

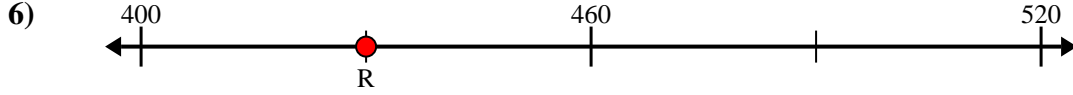


6. _____

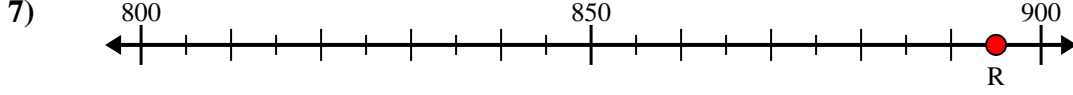


7. _____

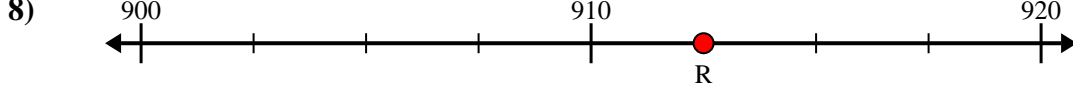

8. _____

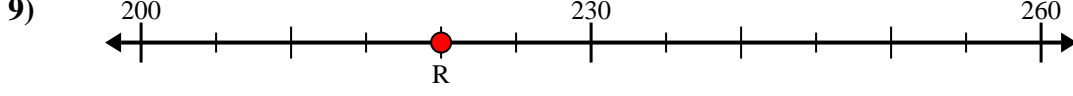











9. _____

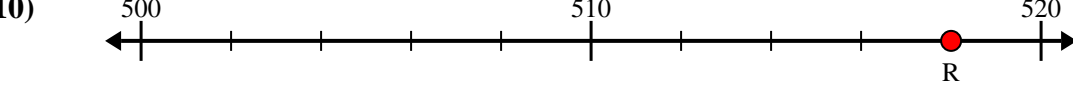

10. _____



Find the value of R.

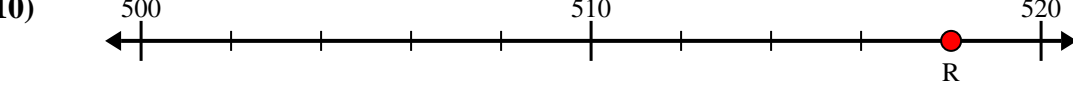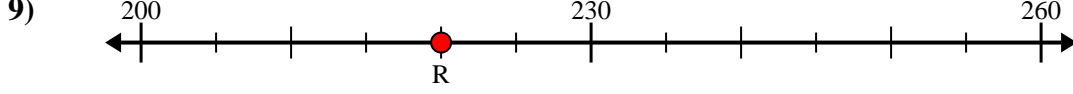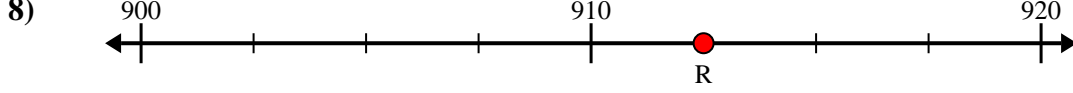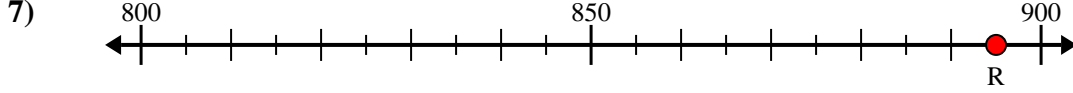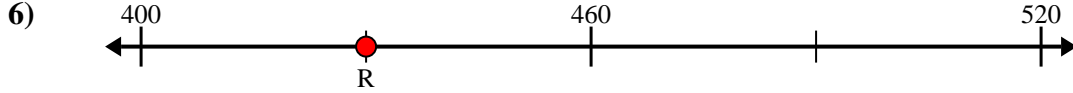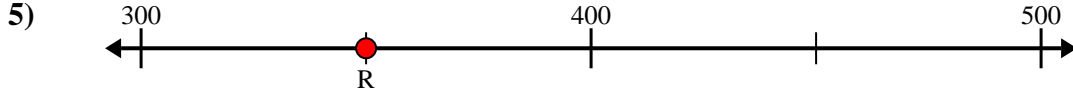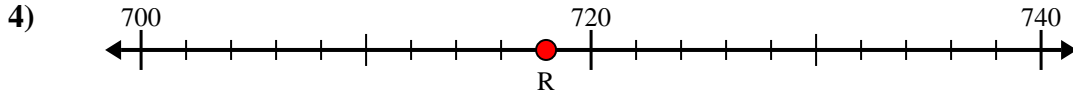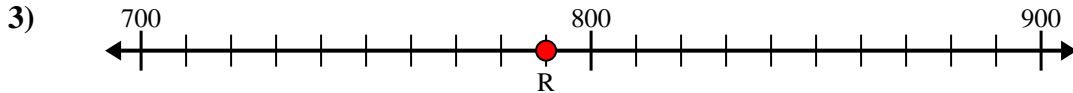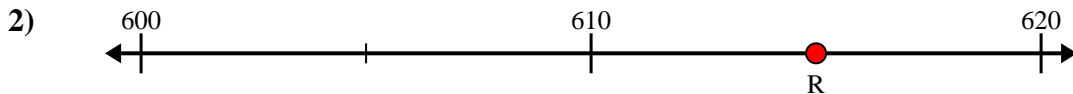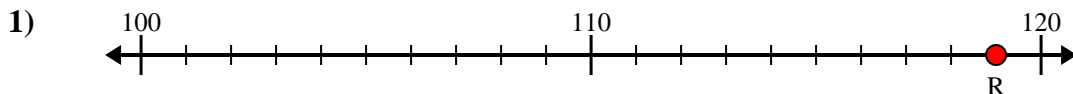

Answers

- 1. 119
- 2. 615
- 3. 790
- 4. 718
- 5. 350
- 6. 430
- 7. 895
- 8. 913
- 9. 220
- 10. 518