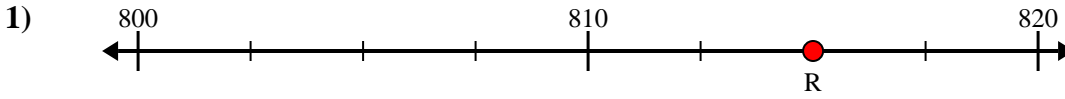





Find the value of R.


Answers




1. _____

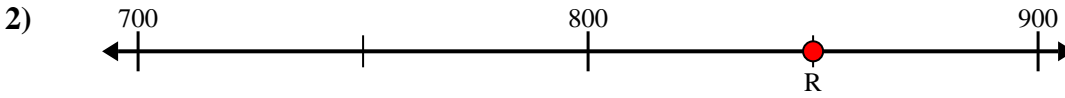


2. _____

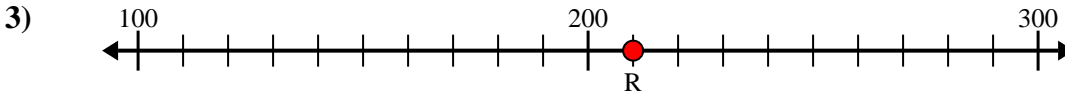


3. _____

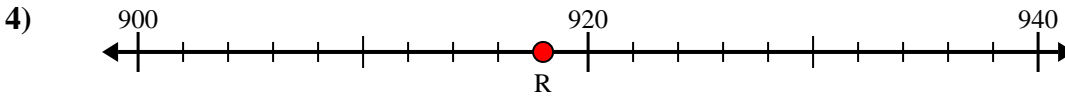


4. _____

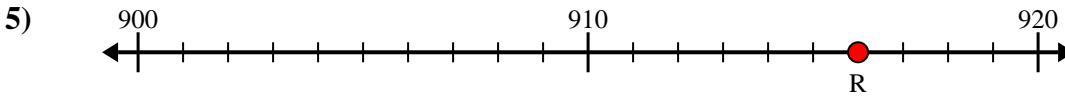


5. _____

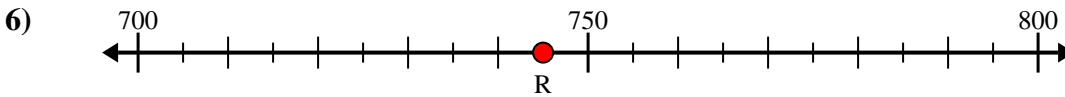


6. _____

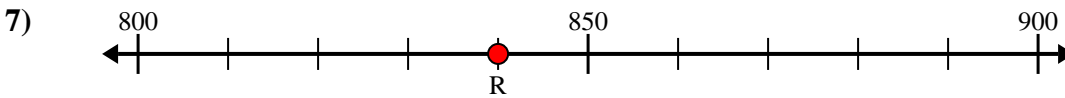


7. _____

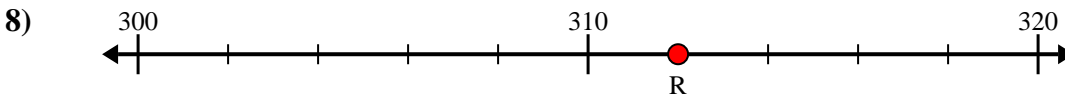

8. _____

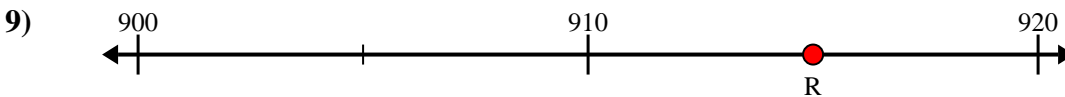











9. _____

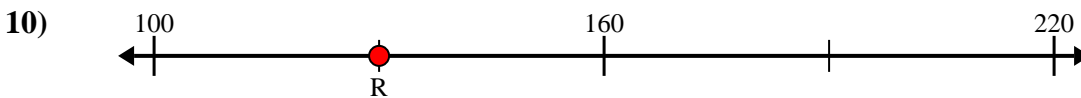

10. _____



Find the value of R.

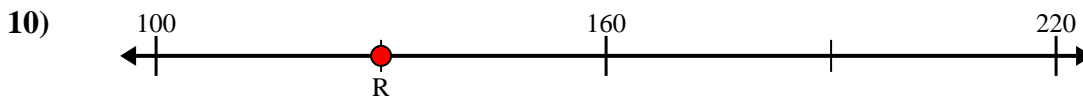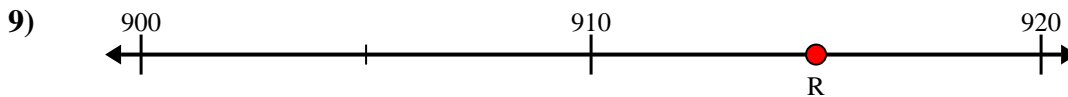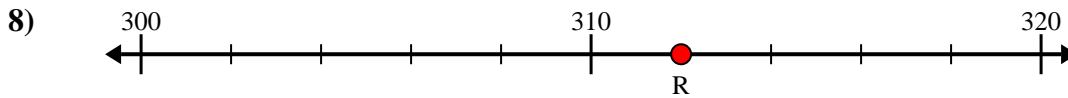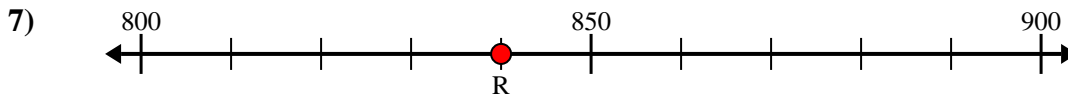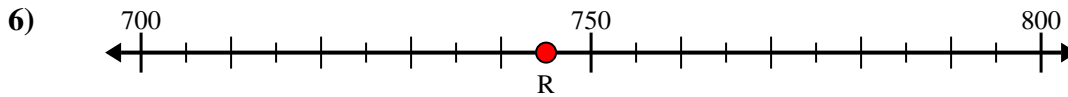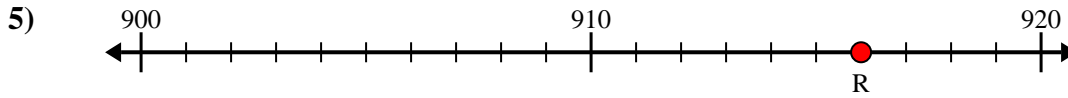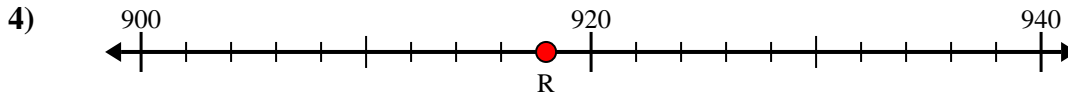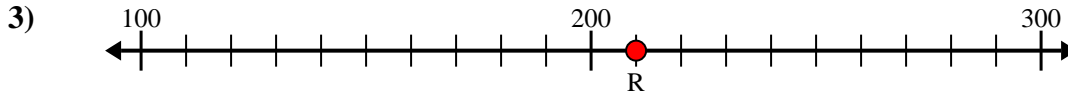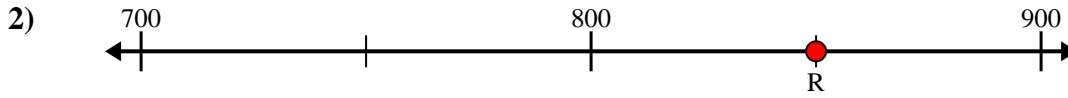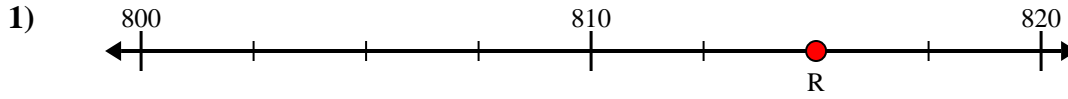

Answers

1. 815

2. 850

3. 210

4. 918

5. 916

6. 745

7. 840

8. 312

9. 915

10. 130