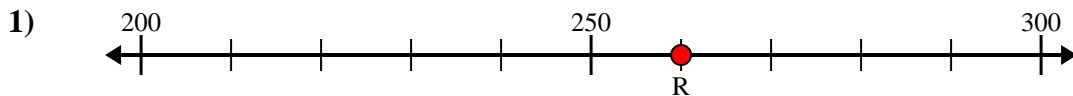





Find the value of R.


Answers




1. \_\_\_\_\_

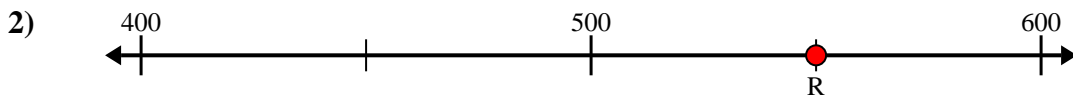

2. \_\_\_\_\_

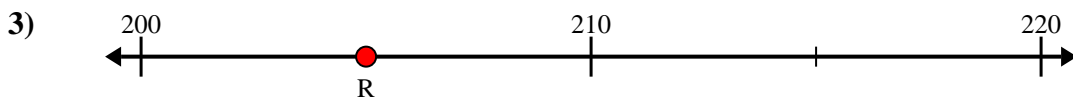


3. \_\_\_\_\_

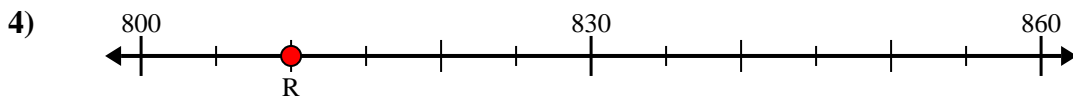


4. \_\_\_\_\_




5. \_\_\_\_\_

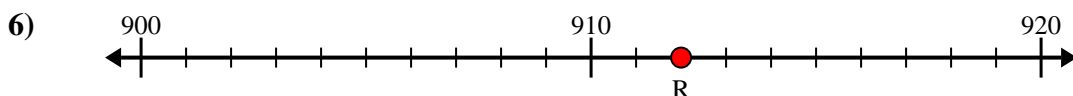


6. \_\_\_\_\_

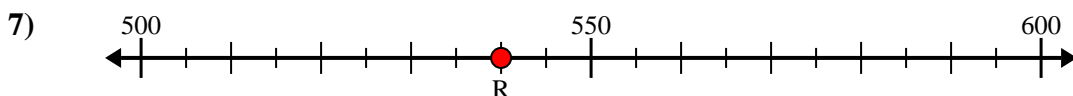


7. \_\_\_\_\_

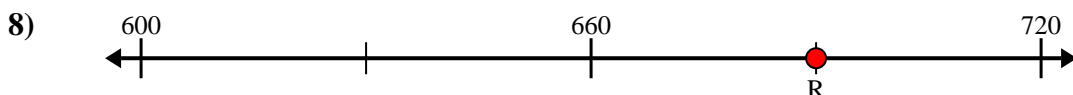

8. \_\_\_\_\_

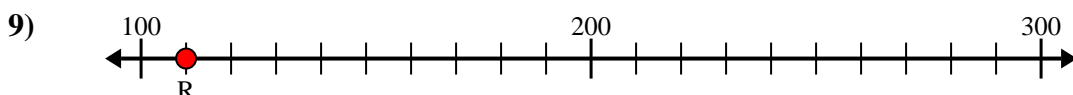










9. \_\_\_\_\_

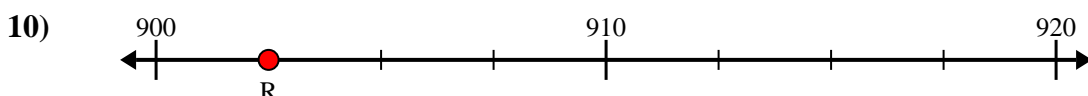

10. \_\_\_\_\_



Find the value of R.

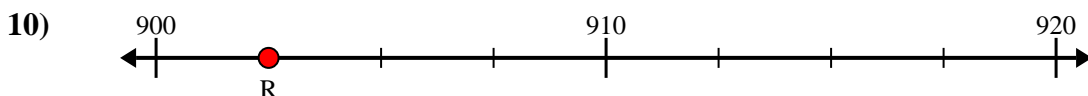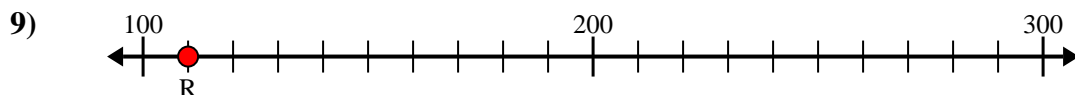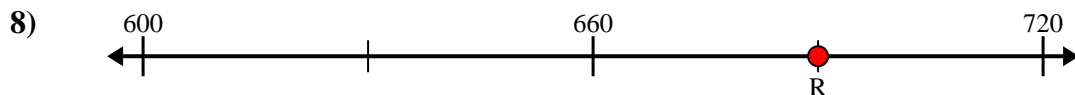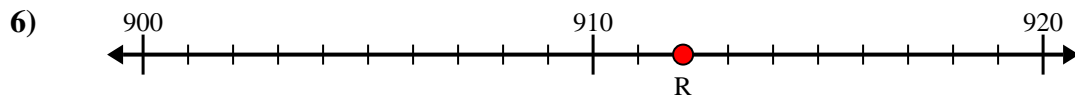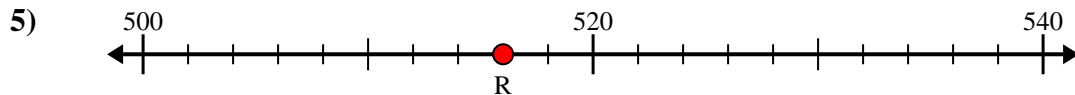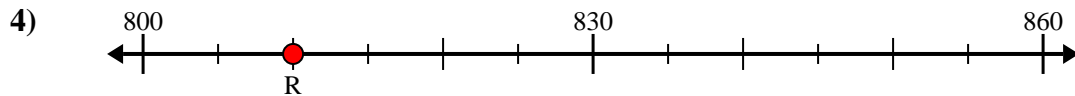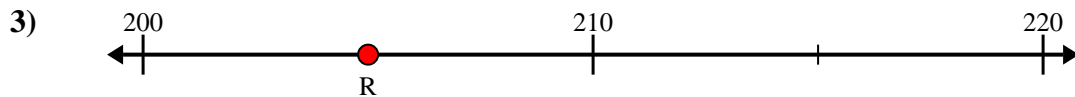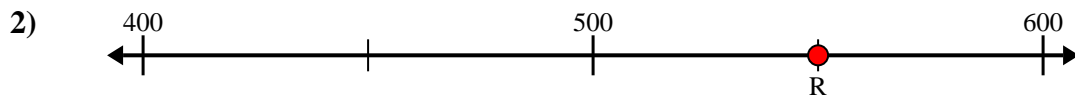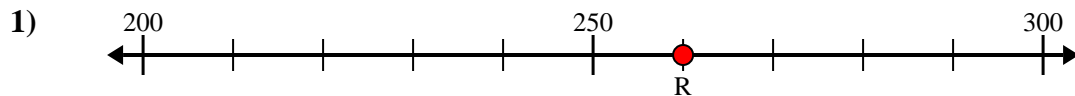

Answers

1. 260

2. 550

3. 205

4. 810

5. 516

6. 912

7. 540

8. 690

9. 110

10. 903