
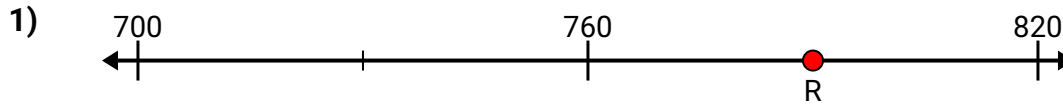


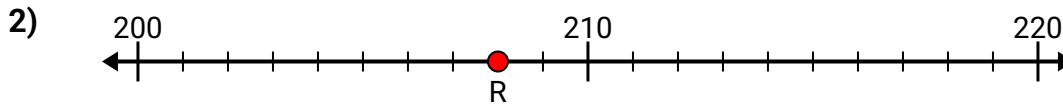


Find the value of R.

Answers


1. _____




2. _____

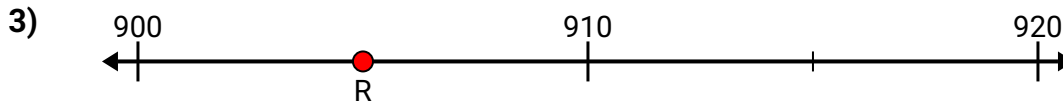


3. _____

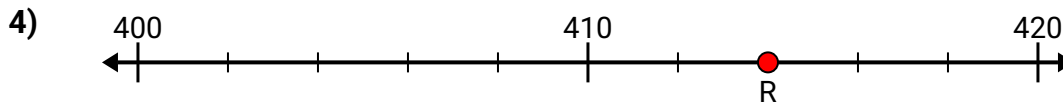


4. _____

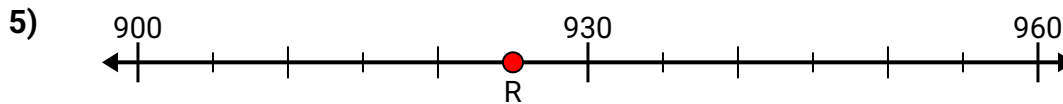


5. _____

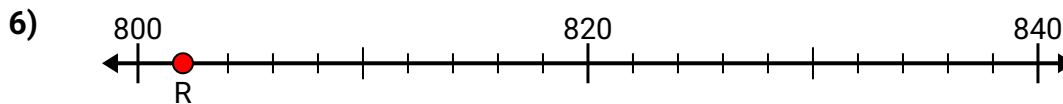


6. _____

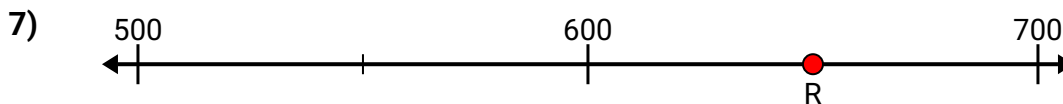


7. _____

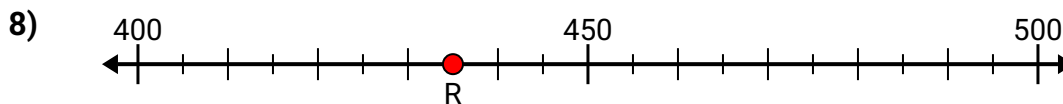

8. _____

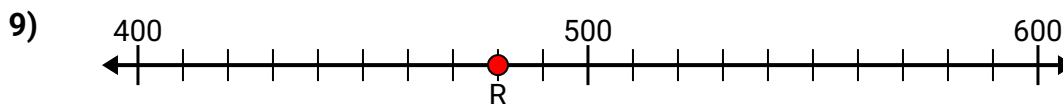











9. _____

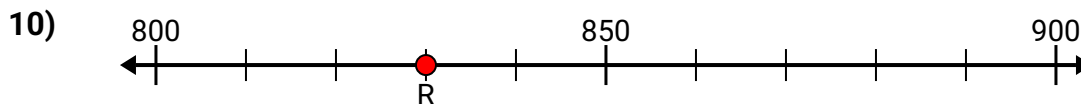

10. _____



Find the value of R.

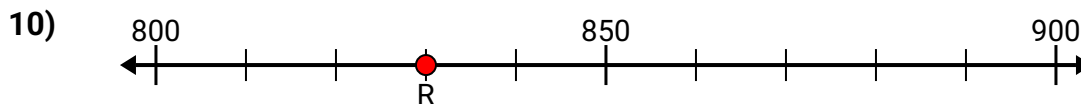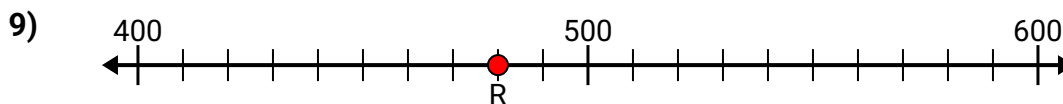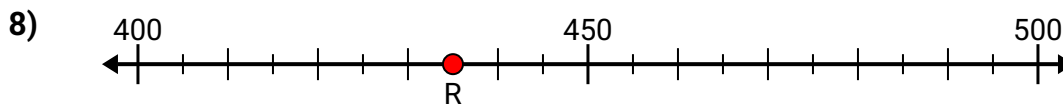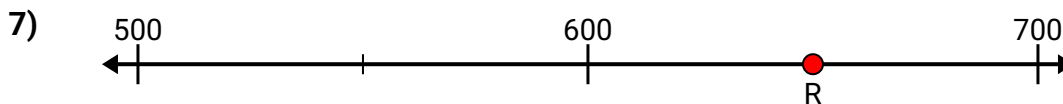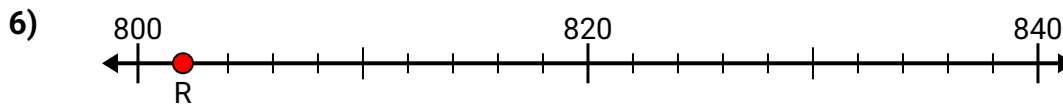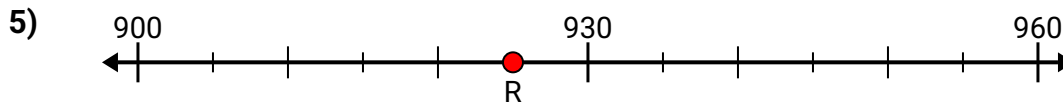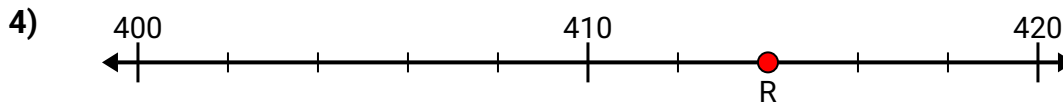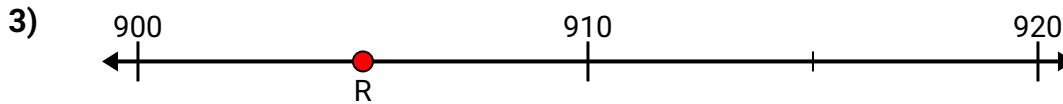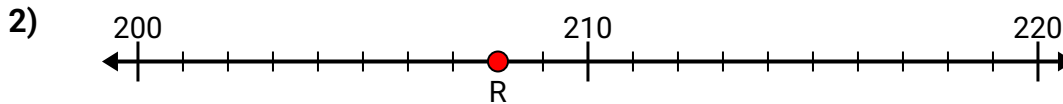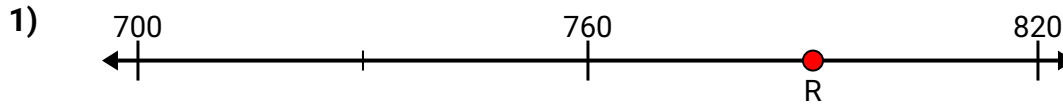**Answers**1. **790**2. **208**3. **905**4. **414**5. **925**6. **802**7. **650**8. **435**9. **480**10. **830**