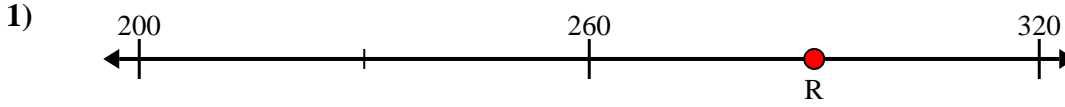





Find the value of R.


Answers




1. _____

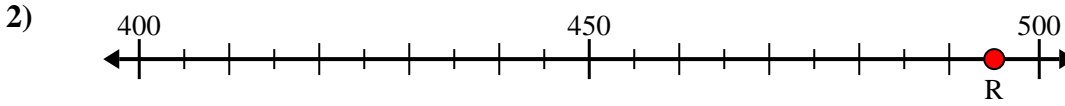


2. _____

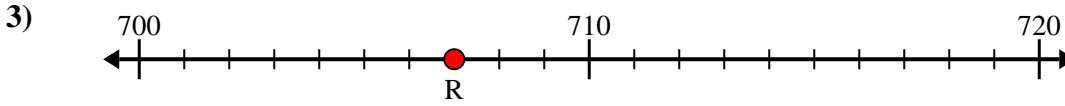


3. _____

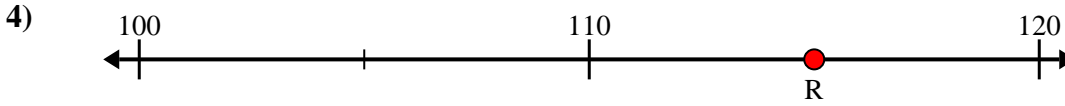


4. _____

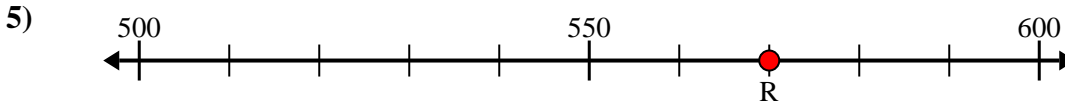


5. _____

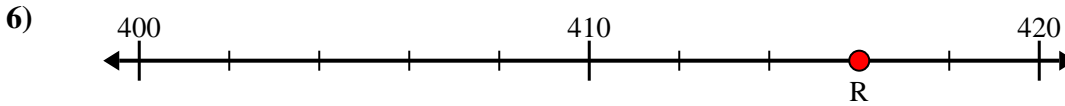

6. _____

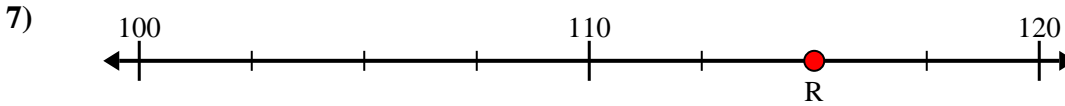


7. _____

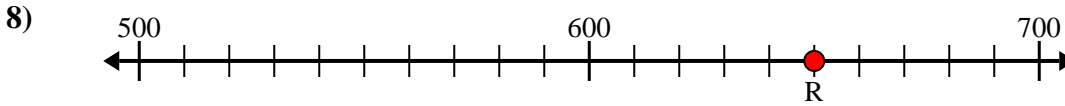

8. _____













9. _____

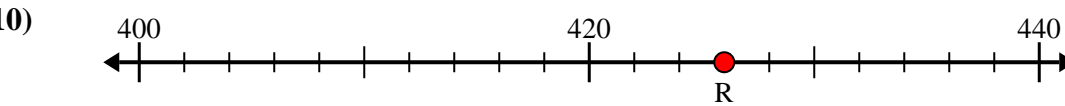

10. _____



Find the value of R.

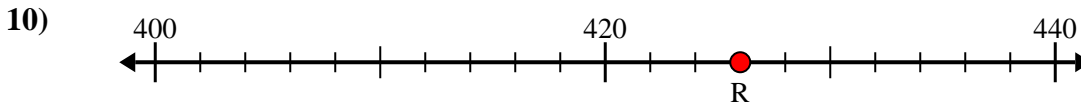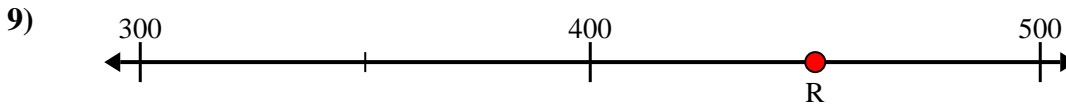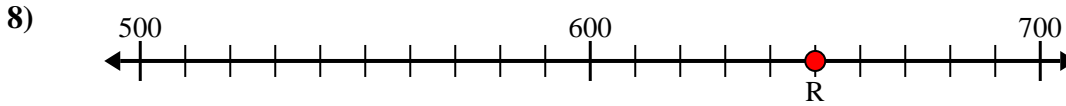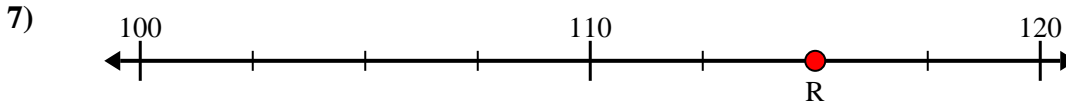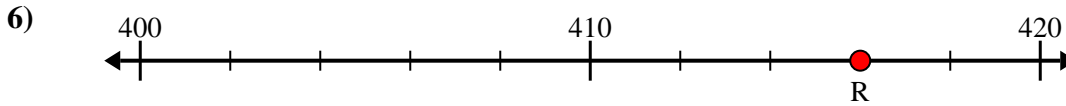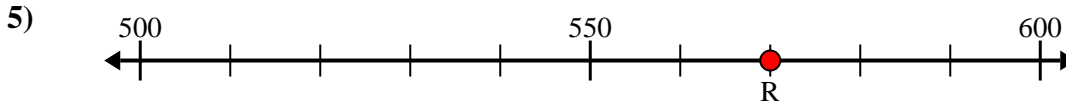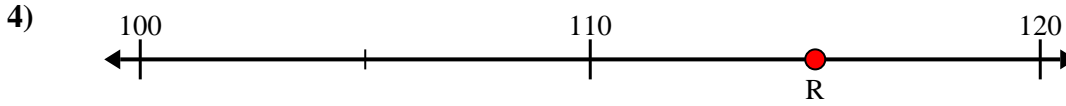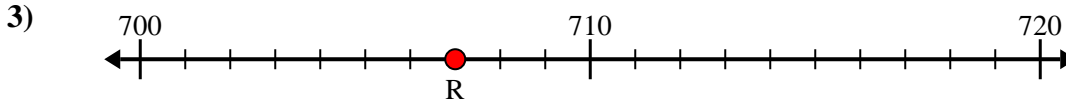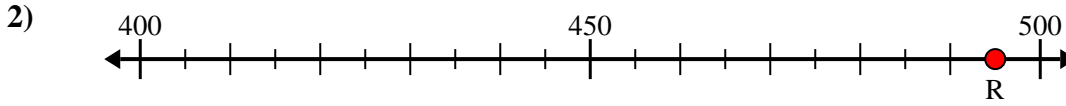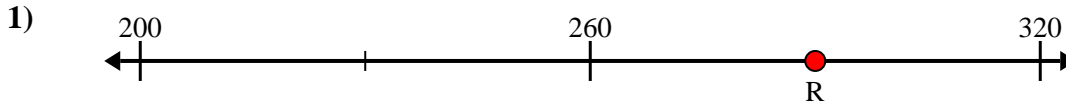

Answers

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650

9. 450

10. 426