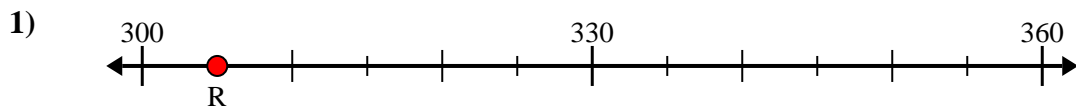





Find the value of R.


Answers




1. \_\_\_\_\_

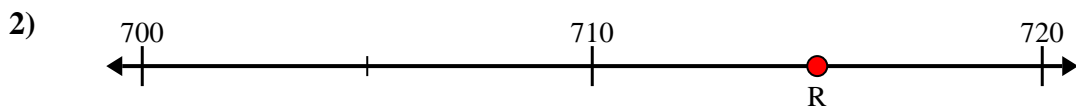


2. \_\_\_\_\_

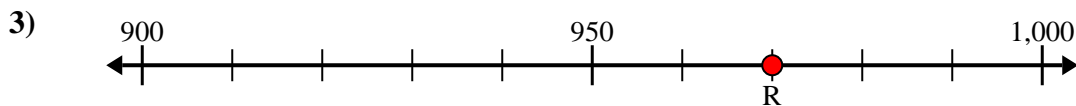


3. \_\_\_\_\_

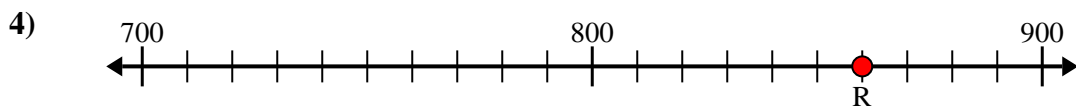


4. \_\_\_\_\_

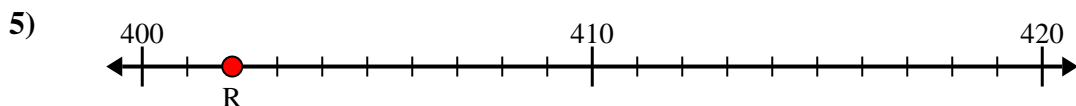


5. \_\_\_\_\_

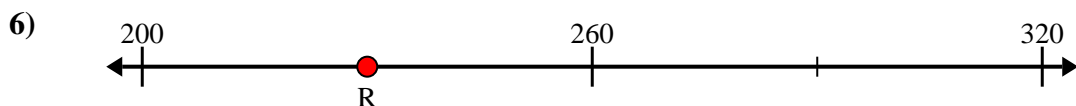


6. \_\_\_\_\_

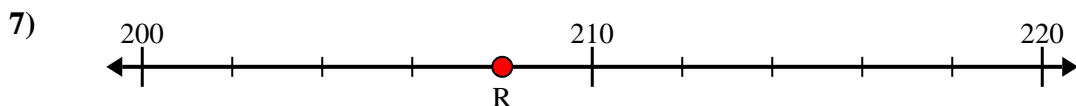


7. \_\_\_\_\_

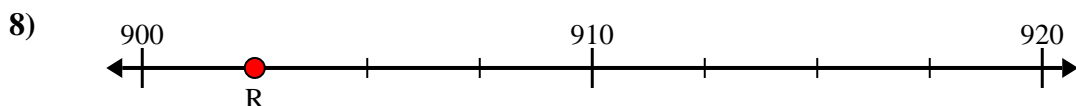

8. \_\_\_\_\_

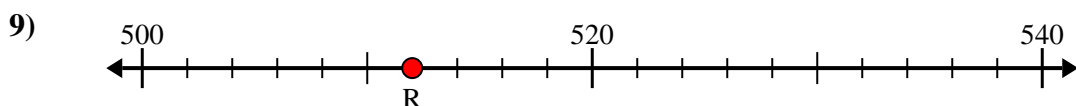











9. \_\_\_\_\_

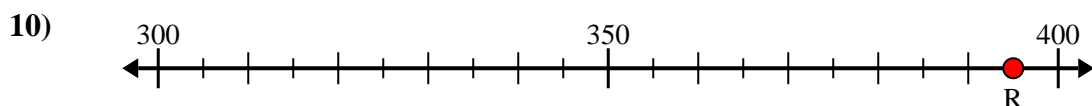

10. \_\_\_\_\_



Find the value of R.

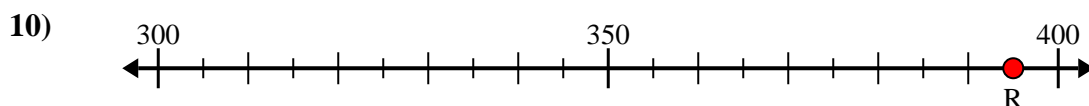       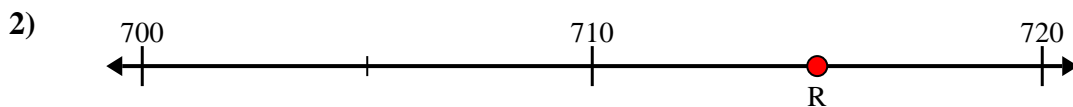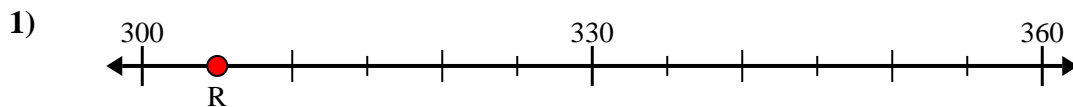

Answers

1. 305

2. 715

3. 970

4. 860

5. 402

6. 230

7. 208

8. 902.5

9. 512

10. 395